

CS152 – Computer Architecture and Engineering

Lecture 2 – Verilog & Multiply Review

2003-08-28

Dave Patterson
(www.cs.berkeley.edu/~patterson)


www-inst.eecs.berkeley.edu/~cs152/



CS 152 L02 Verilog & Multiply Review (1)

Patterson Fall 2003 © UCB

Review: CS 152 roadmap

 

CS 152 L02 Verilog & Multiply Review (2)

Patterson Fall 2003 © UCB

Review

- Continued rapid improvement in Computing
 - 2X every 1.5 years in processor speed;
 - every 2.0 years in memory size;
 - every 1.0 year in disk capacity;
 - Moore's Law enables processor, memory (2X transistors/chip/ ~1.5 yrs)
- 5 classic components of all computers
 - Control
 - Datapath
 - Memory
 - Input
 - Output



Processor



CS 152 L02 Verilog & Multiply Review (3)

Patterson Fall 2003 © UCB

Verilog

- 1 of 2 popular Hardware Description Languages (other is VHDL)
- A language for describing and testing logic circuits.
 - text based way to talk about designs
 - easier to simulate before silicon
 - translate into silicon directly
- No sequential execution, normally hardware just "runs" continuously.
- Verilog: A strange version of C, with some changes to account for time



CS 152 L02 Verilog & Multiply Review (4)

Patterson Fall 2003 © UCB

Overview

- Behavioral vs. Structural Verilog
- Time in Verilog and wave forms
- Testing and Test Benches in Verilog
- Nice online tutorial:
www.eg.bucknell.edu/~cs320/1995-fall/verilog-manual.html



CS 152 L02 Verilog & Multiply Review (5)

Patterson Fall 2003 © UCB

Verilog

- Verilog description composed of modules:

```
module Name ( port list );  
    Declarations and Statements;  
endmodule;
```
- Modules can have instantiations of other modules, or use primitives supplied by language
- Note that Verilog varies from C syntax, borrowing from Ada programming language at times (endmodule)



CS 152 L02 Verilog & Multiply Review (6)

Patterson Fall 2003 © UCB

Verilog

° Verilog has 2 basic modes

1. **Structural composition**: describes that structure of the hardware components, including how ports of modules are connected together

- module contents are built-in gates (and, or, xor, not, nand, nor, xnor, buf) or other modules previously declared

2. **Behavioral**: describes what should be done in a module

- module contents are C-like assignment statements, loops




CS 152 L02 Verilog & Multiply Review (7)

Patterson Fall 2003 © UCB

 Example: Structural XOR (xor built-in, but..)

```
module xor(Z, X, Y);
  input X, Y;
  output Z;
  wire notX, notY, XnotY, YnotX;
  not
    (notX, X),
    (notY, Y);
  or
    (Z, YnotX, XnotY);
  and
    (YnotX, notX, Y),
    (XnotY, X, notY);
endmodule
```



Note: order of gates doesn't matter, since structure determines relationship



CS 152 L02 Verilog & Multiply Review (8)

Patterson Fall 2003 © UCB

Example: Behavioral XOR in Verilog

```
module xorB(Z, X, Y);
  input X, Y;
  output Z;
  reg Z;
  always @ (X or Y)
    Z = X ^ Y; // ^ is C operator for xor
endmodule;
```

° Unusual parts of above Verilog

- “always @ (X or Y)” => whenever X or Y changes, do the following statement
- “reg” is only type of behavioral data that can be changed in assignment, so must redeclare Z as reg



CS 152 L02 Verilog & Multiply Review (9)

- Default is single bit data types: X, Y, Z

Patterson Fall 2003 © UCB

Verilog: replication, hierarchy

° Often in hardware need many copies of an item, connected together in a regular way

- Need way to name each copy
- Need way to specify how many copies

° Specify a module with 4 XORs using existing module example




CS 152 L02 Verilog & Multiply Review (10)

Patterson Fall 2003 © UCB

 Example: Replicated XOR in Verilog

```
module 4xor(C, A, B);
  input [3:0] A, B;
  output [3:0] C;
  xor foo4xor[3:0]
    (.X(A), .Y(B), .Z(C));
endmodule;
```



° Note 1: can associate ports explicitly by name,

- (.X(A), .Y(B), .Z(C))

° or implicitly by order (as in C)

- (C, A, B)

° Note 2: must give a name to new instance of xors (foo4xor)



CS 152 L02 Verilog & Multiply Review (11)

Patterson Fall 2003 © UCB

Verilog big idea: Time in code

° Difference from normal prog. lang. is that time is part of the language

- part of what trying to describe is when things occur, or how long things will take

° In both structural and behavioral Verilog, determine time with #n: event will take place in n time units

- structural: not #2 (notX, X) says notX does not change until time advances 2 ns
- behavioral: #2 Z = A ^ B; says Z does not change until time advances 2 ns

- Default unit is nanoseconds; can change



CS 152 L02 Verilog & Multiply Review (12)

Patterson Fall 2003 © UCB

Example:


```
module test(stream);
  output stream;
  reg stream;
  initial
  begin
    stream = 0;
    #2 stream = 1;
    #5 stream = 0;
    #3 stream = 1;
    #4 stream = 0;
  end
endmodule
```

◦ “Initial” means do this code once

◦ Note: Verilog uses begin ... end vs. { ... } as in C

◦ #2 stream = 1 means wait 2 ns before changing stream to 1

◦ Output called a “waveform”

 


Time and updates

◦ When do assignments take place with respect to \$time?

◦ At next update of clock

Time, variable update, and monitor

or #2 (Z, X, Y);

 

◦ The instant before the rising edge of the clock, all outputs and wires have their OLD values. This includes inputs to flip flops. Therefore, if you change the inputs to a flip flop at a particular rising edge, that change will not be reflected at the output until the NEXT rising edge. This is because when the rising edge occurs, the flip flop still sees the old value. So when simulated time changes in Verilog, then ports, registers updated

Testing in Verilog

◦ Code above just defined a new module

◦ Need separate code to test the module (just like C/Java)

◦ Since hardware is hard to build, major emphasis on testing in HDL

◦ Testing modules called “test benches” in Verilog;

• like a bench in a lab dedicated to testing

◦ Can use time to say how things change

Administrivia

◦ Prerequisite Quiz Friday

1. 11 AM - 1 PM 320 Soda (John)
2. 2 PM - 4 PM 4 Evans (Kurt)
3. 3 PM - 5 PM 81 Evans (Jack)

◦ Lab 1 due next Wednesday (Mon. holiday)

◦ Tuesday: buy \$37 PRS Transmitter from behind ASUC textbook desk (Chem 1A, CS 61ABC, 160)

• Can sell back to bookstore



Example Verilog Code

```
//Test bench for 2-input multiplexor.
// Tests all input combinations.
module testmux2;
  reg [2:0] c;
  wire f;
  reg expected;
  mux2 myMux (.select(c[2]), .in0(c[0]),
    .in1(c[1]), .out(f));
  initial
  begin
    c = 3'b000; expected=1'b0; ...
```

• Verilog constants syntax N'Bxxx where

N is size of constant in bits

B is base: b for binary, h for hex, o for octal
xxx are the digits of the constant

Example Verilog Code

```
... begin
  c = 3'b000; expected=1'b0;
  repeat (7)
    begin
      #10 c = c + 3'b001;
      if (c[2]) expected=c[1];
      else expected=c[0];
    end
  #10 $finish;
end
```

- Verilog if statement, for and while loops like C
 - repeat (n) loops for n times (restricted for)
 - forever is an infinite loop
- Can select a bit of variable (c[0])
- \$finish ends simulation



CS 152 L02 Verilog & Multiply Review (19)

Patterson Fall 2003 © UCB

Rising and Falling Edges and Verilog

◦ Challenge of hardware is when do things change relative to clock?

- Rising clock edge? ("positive edge triggered")
- Falling clock edge? ("negative edge triggered")
- When reach a logical level? ("level sensitive")

◦ Verilog must support any "clocking methodology"

◦ Includes events "posedge", "negedge" to say when clock edge occur, and "wait" statements for level



CS 152 L02 Verilog & Multiply Review (20)

Patterson Fall 2003 © UCB

Verilog Odds and Ends

- Memory is register with second dimension
reg [31:0] memArray [0:255];
- Can assign to group on Left Hand Side
{Cout, sum} = A + B + Cin;
- Can connect logical value 0 or 1 to port via supply0 or supply1
- If you need some temporary variables (e.g., for loops), can declare them as integer
- Since variables declared as number of bits, to place a string need to allocate 8 * number of characters
reg [1 : 6*8] Msg;
Msg = "abcdef";



CS 152 L02 Verilog & Multiply Review (21)

Patterson Fall 2003 © UCB

Blocking v. Nonblocking assignment

- Blocking assignment statement (= operator) like in traditional programming languages
 - The whole statement is done before control passes on to the next statement.
- Non-blocking (<= operator) evaluates all right-hand sides for current time unit and assigns left-hand sides at the end of the time unit
 - Use old values of variables at beginning of current time unit and to assign registers new values at end of current time unit. This reflects how register transfers occur in some hardware systems.



CS 152 L02 Verilog & Multiply Review (22)

Patterson Fall 2003 © UCB

Blocking v. Nonblocking Example

```
// testing blocking and non-blocking assignment
module blocking;
  reg [0:7] A, B;
  initial begin: init1
    A = 3;
    #1 A = A + 1; // blocking procedural assignment
    B = A + 1;
    $display("Blocking: A= %b B= %b", A, B);

    A = 3;
    #1 A <= A + 1; // non-blocking procedural assignment
    B <= A + 1;

    #1 $display("Non-blocking: A= %b B= %b", A, B);
  end
endmodule
```

◦ Above module produces the following output:

```
Blocking: A= 00000100 B= 00000101
Non-blocking: A= 00000100 B= 00000100
```



CS 152 L02 Verilog & Multiply Review (23)

Patterson Fall 2003 © UCB

Peer Instruction

◦ How many mistakes in this module?

```
module test(X);
  output X;
  initial
    begin
      X = 0;
      X = 1;
    end;
end;
```

- A. None
- B. 1
- C. 2
- D. 3
- E. 4
- F. >=5



CS 152 L02 Verilog & Multiply Review (24)

Patterson Fall 2003 © UCB

Peer Instruction

- How many mistakes in this module?

```
module test2(X);
  output X; reg X; // so can change
  initial
  begin
    X = 0;
    #2 X = 1; // no time delay
  end // no ;
endmodule_ // Ada style end, and no ;
```

- A. None D. 3
B. 1 E. 4
C. 2 F. **>=5**

Peer Instruction

- Suppose writing a MIPS interpreter in Verilog. Which sequence below is best organization for the interpreter?

- A repeat loop that fetches instructions
- A while loop that fetches instructions
- Increments PC by 4
- Decodes instructions using case statement
- Decodes instr. using chained if statements
- Executes each instruction

- A. I, IV, VI D. IV, VI, III, II
B. II, III, IV, VI E. V, VI, III, I
C. I, V, VI, III F. VI, III, II

Peer Instruction

- Suppose writing a MIPS interpreter in Verilog. Which sequence below is best organization for the interpreter?

- A repeat loop that fetches instructions
- A while loop that fetches instructions
- Increments PC by 4
- Decodes instructions using case statement
- Decodes instr. using chained if statements
- Executes each instruction

- A. I, IV, VI D. IV, VI, III, II
B. II, III, IV, VI E. V, VI, III, I
C. I, V, VI, III F. VI, III, II

Verilog conclusion

- Verilog allows both structural and behavioral descriptions, helpful in testing
- Syntax a mixture of C (operators, for, while, if, print) and Ada (begin... end, case...endcase, module ...endmodule)
- Some special features only in Hardware Description Languages
 - # time delay, initial vs. always, forever loops
- Verilog can describe everything from single gate to full computer system; you get to design a simple processor

MIPS arithmetic instructions

Instruction	Example	Meaning	Comments
add	add \$1,\$2,\$3	\$1 = \$2 + \$3	3 operands; exception possible
subtract	sub \$1,\$2,\$3	\$1 = \$2 - \$3	3 operands; exception possible
add immediate	addi \$1,\$2,100	\$1 = \$2 + 100	+ constant; exception possible
add unsigned	addu \$1,\$2,\$3	\$1 = \$2 + \$3	3 operands; no exceptions
subtract unsigned	subu \$1,\$2,\$3	\$1 = \$2 - \$3	3 operands; no exceptions
add imm. unsign.	addiu \$1,\$2,100	\$1 = \$2 + 100	+ constant; no exceptions
multiply	mult \$2,\$3	Hi, Lo = \$2 x \$3	64-bit signed product
multiply unsigned	multu \$2,\$3	Hi, Lo = \$2 x \$3	64-bit unsigned product
divide	div \$2,\$3	Lo = \$2 ÷ \$3, Hi = \$2 mod \$3	Lo = quotient, Hi = remainder
divide unsigned	divu \$2,\$3	Lo = \$2 ÷ \$3, Hi = \$2 mod \$3	Unsigned quotient &
remainder			
Move from Hi	mghi \$1	\$1 = Hi	Used to get copy of Hi
Move from Lo	mfllo \$1	\$1 = Lo	Used to get copy of Lo

MULTIPLY (unsigned)


- Paper and pencil example (unsigned):

```

Multiplicand    1000
Multiplier      1001
-----
1000
0000
0000
1000
Product        01001000
```

- m bits x n bits = m+n bit product
- Binary makes it easy:
 - 0 => place 0 (0 x multiplicand)
 - 1 => place a copy (1 x multiplicand)
- 4 versions of multiply hardware & algorithm:
 - successive refinement


Unsigned Combinational Multiplier

 

° Stage i accumulates $A * 2^i$ if $B_i == 1$

° Q: How much hardware for 32 bit multiplier? Critical path?


How does it work?

 

- ° At each stage shift A left ($\times 2$)
- ° Use next bit of B to determine whether to add in shifted multiplicand
- ° Accumulate $2n$ bit partial product at each stage


Unsigned shift-add multiplier (version 1)

 ° 64-bit Multiplicand reg, 64-bit ALU, 64-bit Product reg, 32-bit multiplier reg



Multiplier = datapath + control

Multiply Algorithm Version 1

 

Product Multiplier Multiplier

0000 0000 0011 0000 0010
1: 0000 0010 0011 0000 0010
2: 0000 0010 0011 0000 0100
3: 0000 0010 0001 0000 0100
1: 0000 0110 0001 0000 0100
2: 0000 0110 0001 0000 1000
3: 0000 0110 0000 0000 1000
0000 0110 0000 0000 1000


Observations on Multiply Version 1

- ° 1 clock per cycle $\Rightarrow \approx 100$ clocks per multiply
 - Ratio of multiply to add 5:1 to 100:1
- ° 1/2 bits in multiplicand always 0 $\Rightarrow$ 64-bit adder is wasted
- ° 0's inserted in right of multiplicand as shifted $\Rightarrow$ least significant bits of product never changed once formed

° Instead of shifting multiplicand to left, shift product to right?


MULTIPLY HARDWARE Version 2

 ° 32-bit Multiplicand reg, 32-bit ALU, 64-bit Product reg, 32-bit Multiplier reg




How to think of this?

 Remember original combinational multiplier:




Simply warp to let product move right...

 


° Multiplicand stay's still and product moves right

Multiply Algorithm Version 2

 

Still more wasted space!

 


Observations on Multiply Version 2


° Product register wastes space that exactly matches size of multiplier
=> combine Multiplier register and Product register

MULTIPLY HARDWARE Version 3

 ° 32-bit Multiplicand reg, 32-bit ALU, 64-bit Product reg, (0-bit Multiplier reg)



Multiply Algorithm Version 3

 

Observations on Multiply Version 3

- 2 steps per bit because Multiplier & Product combined
- MIPS registers Hi and Lo are left and right half of Product
- Gives us MIPS instruction MultU



In Conclusion...

- Multiply: successive refinement to see final design
 - 32-bit Adder, 64-bit shift register, 32-bit Multiplicand Register
 - There are algorithms that calculate many bits of multiply per cycle (see exercises 4.36 to 4.39 in COD)

