

CS152 – Computer Architecture and Engineering

Lecture 8 – Logic Review

2003-09-18

Dave Patterson

(www.cs.berkeley.edu/~patterson)

www-inst.eecs.berkeley.edu/~cs152/

Review

• Single cycle datapath => CPI=1, CCT => long

• 5 steps to design a processor

1. Analyze instruction set => datapath requirements
2. Select set of datapath components & establish clock methodology
3. Assemble datapath meeting the requirements
4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
5. Assemble the control logic


• Control is the hard part

• MIPS makes control easier

- Instructions same size
- Source registers always in same place
- Immediate same size, location
- Operations always on registers/immediates

• On-line Design Notebook

 - Open a window and keep an editor running while you work; cut&paste
- Former CS 152 students (and TAs) say they use on-line notebook for programming as well as hardware design; one of most valuable skills
- Refer to the handout as an example



CS 152 L08 Logic Design Review (1)

Patterson Fall 2003 © UCB




CS 152 L08 Logic Design Review (2)

Patterson Fall 2003 © UCB

Outline

- Combinational Logic + Verilog Representation
- FlipFlops, Registers + Verilog Representation
- FSM + Verilog Representation
- Implementation of Control Representation of Single Cycle Datapath

General Model of a Synchronous Circuit

 

- All wires, except clock, may be multiple bits wide.
- Registers (reg)
 - collections of flip-flops
- clock
 - distributed to all flip-flops
- Combinational Logic Blocks (CL)
 - no internal state
 - output only a function of inputs
- Particular inputs/outputs are optional
- Optional Feedback



CS 152 L08 Logic Design Review (3)


Patterson Fall 2003 © UCB



CS 152 L08 Logic Design Review (4)

Patterson Fall 2003 © UCB

Combinational Logic (CL) Defined

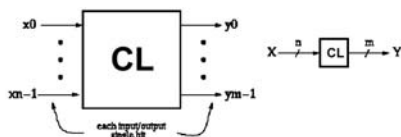

$$y_i = f_i(x_0, \dots, x_{n-1}), \text{ where } x, y \text{ are } \{0,1\}.$$

Y is a function of only X.

- If we change X, Y will change immediately (well almost!).
- There is an implementation dependent delay from X to Y.

Some Combinational Logic Pieces

• OR gates

• AND gates

• NAND gates

• NOR gates

• XOR gates

• XNOR gates

• NOT gates

• Etc....

• Multiplexor



If s=1 then c=a else c=b



CS 152 L08 Logic Design Review (5)

Patterson Fall 2003 © UCB




CS 152 L08 Logic Design Review (6)

Patterson Fall 2003 © UCB

Verilog Representation

$$\text{Cout} = a \cdot b + b \cdot \text{cin} + a \cdot \text{cin}$$

$$S = a \text{ xor } b \text{ xor } c$$

 

```
module FA(a, b, cin, cout, s)
```

```
  Input a, b, cin;
```

```
  Output cout, s;
```

```
  wire cout, s;
```

```
  assign cout = a & b + b & cin + a & cin;
```

```
  assign s = a ^ b ^ cin;
```

```
endmodule
```

•Why are cout and s wires?


•Notice there is no clock in this code

•Why use "assign ... =" ?

Alternative Verilog Representation

$$\text{Cout} = a \cdot b + b \cdot \text{cin} + a \cdot \text{cin}$$

$$S = a \text{ xor } b \text{ xor } c$$

 

```
module FA(a, b, cin, cout, s)
```

```
  Input a, b, cin;
```

```
  output cout, s;
```

```
  Reg cout, s;
```

```
  always@(a or b or cin) begin
```

```
    if ( (a && b) || (b && cin) || (a && cin) )
```

```
      cout <= 1;
```

```
    else
```

```
      cout <= 0;
```

```
    s <= a ^ b ^ cin;
```

```
  end
```

```
endmodule
```

•What's the difference between && and &?

•Why are cout and s declared as reg now?

•Notice there is no clock in this code either

Combinational Always Blocks

- Make sure all signals assigned in a combinational always block are explicitly assigned values every time that the always block executes. Otherwise latches will be generated to hold the last value for the signals not assigned values.

- Example:

- Sel case value 2'd2 omitted.
- Out is not updated when select line has 2'd2.
- Latch is added by tool to hold the last value of out under this condition.

```
module mux4to1 (out, a, b, c, d, sel);
  output out;
  input a, b, c, d;
  input [1:0] sel;
  reg out;
  always @(sel or a or b or c or d)
  begin
    case (sel)
      2'd0: out = a;
      2'd1: out = b;
      2'd3: out = d;
    endcase
  end
endmodule
```

Combinational Always Blocks

- To avoid synthesizing a latch in this case, add the missing select line:

```
2'd2: out = c;
```

- Or, in general, use the "default" case:


```
default: out = foo;
```

- If you don't care about the assignment in a case (for instance you know that it will never come up) then assign the value "x" to the variable. Example:


```
default: out = 1'bx;
```

The x is treated as a "don't care" for synthesis and will simplify the logic.

D-type edge-triggered flip-flop

 


 - The edge of the clock is used to sample the "D" input & send it to "Q" (positive edge triggering).
- At all other times the output Q is independent of the input D (just stores previously sampled value).
- The input must be stable for a short time before the clock edge.




FF timing revisited

Delay in Flip-flops

 

- On the posedge, the flip flop will latch in the value sitting on the D side of the flip flop, provided that the input has been stable for the "setup time"
- The actual output of the FF (the "Q") doesn't change until after the clock to Q delay.

Verilog representations of FFs

 

```
reg myReg;
always @(posedge clk) begin
    if (ctr == 1)
        myReg <= B;
    else
        myReg <= A;
end
endmodule
```

•myReg is declared as a reg

•Notice that the only thing in the sensitivity list is "posedge clk". This creates a register

CS 152 L08 Logic Design Review (13)

Patterson Fall 2003 © UCB

Administrivia

- Office hours in Lab
 - Mon 5 – 6:30 Jack, Tue 3:30-5 Kurt,
 - Wed 3 – 4:30 John, Thu 3:30-5 Ben
- Dave's office hours Tue 3:30 – 5
- Lab 3 up
- Reading: Sections 5.6, 5.8, 5.11, 5.12 in Beta ed.
- T.A. Review Design Document with groups in discussion section Friday
- Design Document: Email to TA today 9/17

CS 152 L08 Logic Design Review (14)

Patterson Fall 2003 © UCB


Administrivia: Design Document

- Design Document: 2-4 pages for Lab 3
- Should include:
 - Defining the Problem (makes sure you understand the problem)
 - Approach / Plan of Attack
 - Division of Labor
 - Timeline
 - Basic block diagrams of datapath pieces
 - Skeleton Verilog modules
 - Plan of testing

CS 152 L08 Logic Design Review (15)

Patterson Fall 2003 © UCB


FSM structure

 

CS 152 L08 Logic Design Review (16)

Patterson Fall 2003 © UCB

FSM description

 

CS 152 L08 Logic Design Review (17)

Patterson Fall 2003 © UCB

Verilog Code – FSM State Register

```
module trafficLightFSM(clk, reset, change, red, yellow, green);
    input clk, reset, change;
    output red, yellow, green;
    reg red, yellow, green;
    reg [1:0] curState, nextState;
    parameter showRed = 2'b00, showYellow = 2'b01;
    parameter showGreen = 2'b10;
```

```
// state register
always @(posedge clk)
    if (reset==1'b1) curState <= 2'b0;
    else curState <= nextState;
```

CS 152 L08 Logic Design Review (18)

Patterson Fall 2003 © UCB

FSM Next State Logic

```
// next state logic
// dependent only on the current state and input
always @(curState or change)
begin
    nextState = showRed; // default state
    case (curState)
        showRed: if (change) nextState=showGreen;
        showYellow: if (change) nextState=showRed;
                    else nextState=showYellow;
        showGreen: if (change) nextState=showYellow;
                    else nextState=showGreen;
    endcase
end
```




FSM Output Logic

```
// Output Logic: dependent ONLY on state
always @(curState) begin
    // *ALWAYS* put default output values
    red=1'b0; green=1'b0; yellow=1'b0;
    case (curState)
        showRed: red=1'b1;
        showYellow: yellow=1'b1;
        showGreen: green=1'b1;
    endcase
end
endmodule
```




Verilog: Non-Blocking? Assignments
 
```
always @(posedge clk)
begin
    E <= ~A;
    C <= ~E;
end
```



Verilog: Blocking? Assignments
 
```
always @(posedge clk)
begin
    E = ~A;
    C = ~E;
end
```



A final word on Verilog


- Verilog does not turn hardware design into writing programs!
 - Since Verilog looks similar to programming languages, some think that they can design hardware by writing programs. **NOT SO.**
 - Verilog is a hardware **description** language. The best way to use it is to first figure out the circuit you want, then figure out how to **describe** it in Verilog.
 - The behavioral construct hides a lot of the circuit details but you as the designer must still manage the structure, data-communication, parallelism, and timing of your design. Not doing so leads to **very inefficient designs.**



Peer Instruction



Step 4: Given Datapath: RTL -> Control

 

A Summary of the Control Signals

Sec

Appendix A

func

op

10 0000	10 0010	We Don't Care :-)						
00 0000	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010		
	add	sub	ori	lw	sw	beq	jump	
RegDst	1	1	0	0	x	x	x	
ALUSrc	0	0	1	1	1	0	x	
MemtoReg	0	0	0	1	x	x	x	
RegWrite	1	1	1	1	0	0	0	
MemWrite	0	0	0	0	1	0	0	
PCSrc	0	0	0	0	0	1	0	
Jump	0	0	0	0	0	0	1	
ExtOp	x	x	0	1	1	x	x	
ALUctr<2:0>	Add	Subtract	Or	Add	Add	Subtract	xxx	

312621161160

op	rs	rt	rd	shamt	funct	add, sub
----	----	----	----	-------	-------	----------

I-type


op	rs	rt	immediate			ori, lw, sw, beq
----	----	----	-----------	--	--	------------------

J-type


op	target address				jump
----	----------------	--	--	--	------

The Concept of Local Decoding

op	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	R-type	ori	lw	sw	beq	jump
RegDst	1	0	0	x	x	x
ALUSrc	0	1	1	1	0	x
MemtoReg	0	0	1	x	x	x
RegWrite	1	1	1	0	0	0
MemWrite	0	0	0	1	0	0
Branch	0	0	0	0	1	0
Jump	0	0	0	0	0	1
ExtOp	x	0	1	1	x	x
ALUop<N:0>	"R-type"	Or	Add	Add	Subtract	xxx

 


The Encoding of ALUop

 

- In this exercise, ALUop has to be 2 bits wide to represent:
 - (1) "R-type" instructions
 - "I-type" instructions that require the ALU to perform:
 - (2) Or, (3) Add, and (4) Subtract
- To implement the more of MIPS ISA, ALUop has to be 3 bits to represent:
 - (1) "R-type" instructions
 - "I-type" instructions that require the ALU to perform:
 - (2) Or, (3) Add, (4) Subtract, and (5) And (Example: andi)

ALUop (Symbolic)	R-type	ori	lw	sw	beq	jump
ALUop<2:0>	1 00	0 10	0 00	0 00	0 01	xxx

The Decoding of the "func" Field

 

ALUop (Symbolic)	R-type	ori	lw	sw	beq	jump
ALUop<2:0>	1 00	0 10	0 00	0 00	0 01	xxx

R-type	op	rs	rt	rd	shamt	funct
--------	----	----	----	----	-------	-------

P. 286 text:

func<5:0>	Instruction Operation
10 0000	add
10 0010	subtract
10 0100	and
10 0101	or
10 1010	set-on-less-than

ALUctr<2:0>	ALU Operation
000	And
001	Or
010	Add
110	Subtract
111	Set-on-less-than

The Truth Table for ALUctr

						func<3:0>	Instruction Op.
						0000	add
						0010	subtract
						0100	and
						0101	or
						1010	set-on-less-than

ALUop (Symbolic)	R-type "R-type"	ori	lw	sw	beq
ALUop<2:0>	1 00	0 10	0 00	0 00	0 01

ALUop			func				ALU Operation	ALUctr		
bit<2>	bit<1>	bit<0>	bit<3>	bit<2>	bit<1>	bit<0>		bit<2>	bit<1>	bit<0>
0	0	0	x	x	x	x	Add	0	1	0
0	x	1	x	x	x	x	Subtract	1	1	0
0	1	x	x	x	x	x	Or	0	0	1
1	x	x	0	0	0	0	Add	0	1	0
1	x	x	0	0	1	0	Subtract	1	1	0
1	x	x	0	1	0	0	And	0	0	0
1	x	x	0	1	0	1	Or	0	0	1
1	x	x	1	0	1	0	Set on <	1	1	1

Turn Truth Table into Logic?

- Look at each output signal
- For each signal, subset truth table to include every row of when that signal is 1
- Create logic equations that cover each row, but try to minimize the logic



The Logic Equation for ALUctr<2>

ALUop			func				ALUctr<2>
bit<2>	bit<1>	bit<0>	bit<3>	bit<2>	bit<1>	bit<0>	
0	x	1	x	x	x	x	1
1	x	x	0	0	1	0	1
1	x	x	1	0	1	0	1

This makes func<3> a don't care

- $ALUctr<2> = (!ALUop<2> \& ALUop<0>) + (ALUop<2> \& !func<2> \& func<1> \& !func<0>)$



The Logic Equation for ALUctr<1>

ALUop			func				ALUctr<1>
bit<2>	bit<1>	bit<0>	bit<3>	bit<2>	bit<1>	bit<0>	
0	0	0	x	x	x	x	1
0	x	1	x	x	x	x	1
1	x	x	0	0	0	0	1
1	x	x	0	0	1	0	1
1	x	x	1	0	1	0	1

- $ALUctr<1> = (!ALUop<2> \& !ALUop<1>) + (ALUop<2> \& !func<2> \& !func<0>)$




The Logic Equation for ALUctr<0>

ALUop			func				ALUctr<0>
bit<2>	bit<1>	bit<0>	bit<3>	bit<2>	bit<1>	bit<0>	
0	1	x	x	x	x	x	1
1	x	x	0	1	0	1	1
1	x	x	1	0	1	0	1

- $ALUctr<0> = (!ALUop<2> \& ALUop<1>) + (ALUop<2> \& !func<3> \& func<2> \& !func<1> \& func<0>) + (ALUop<2> \& func<3> \& !func<2> \& func<1> \& !func<0>)$



The ALU Control Block

 

- $ALUctr<2> = !ALUop<2> \& ALUop<0> + ALUop<2> \& !func<2> \& func<1> \& !func<0>$
- $ALUctr<1> = !ALUop<2> \& !ALUop<1> + ALUop<2> \& !func<2> \& !func<0>$
- $ALUctr<0> = !ALUop<2> \& ALUop<1> + ALUop<2> \& !func<3> \& func<2> \& !func<1> \& func<0> + ALUop<2> \& func<3> \& !func<2> \& func<1> \& !func<0>$



Step 5: Logic for each control signal


- $PCSrc \leq (OP == 'BEQ) ? 'Br : 'plus4;$
- $ALUsrc \leq (OP == 'Rtype) ? 'regB : 'immed;$
- $ALUctr \leq (OP == 'Rtype) ? 'func : (OP == 'ORI) ? 'ORfunction : (OP == 'BEQ) ? 'SUBfunction : 'ADDfunction;$
- $ExtOp \leq \underline{\hspace{2cm}}$
- $MemWr \leq \underline{\hspace{2cm}}$
- $MemtoReg \leq \underline{\hspace{2cm}}$
- $RegWr \leq \underline{\hspace{2cm}}$
- $RegDst \leq \underline{\hspace{2cm}}$



Step 5: Logic for each control signal

- PCSrc <= (OP == `BEQ) ? `Br : `plus4;
- ALUSrc <= (OP == `Rtype) ? `regB : `immed;
- ALUctr <= (OP == `Rtype) ? `func :
(OP == `ORI) ? `ORfunction :
(OP == `BEQ) ? `SUBfunction : `ADDfunction;
- ExtOp <= (OP == `ORI) ? `ZEROextend : `SIGNextend;
- MemWr <= (OP == `Store) ? 1 : 0;
- MemtoReg <= (OP == `Load) ? 1 : 0;
- RegWr: <= ((OP == `Store) || (OP == `BEQ)) ? 0 : 1;
- RegDst: <= ((OP == `Load) || (OP == `ORI)) ? 0 : 1;

The "Truth Table" for the Main Control

 


op	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	R-type	ori	lw	sw	beq	jump
RegDst	1	0	0	x	x	x
ALUSrc	0	1	1	1	0	x
MemtoReg	0	0	1	x	x	x
RegWrite	1	1	1	0	0	0
MemWrite	0	0	0	1	0	0
PCSrc	0	0	0	0	1	0
Jump	0	0	0	0	0	1
ExtOp	x	0	1	1	x	x
ALUop (Symbolic)	"R-type"	Or	Add	Add	Subtract	xxx
ALUop <2>	1	0	0	0	0	x
ALUop <1>	0	1	0	0	0	x
ALUop <0>	0	0	0	0	1	x


The "Truth Table" for RegWrite

op	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	R-type	ori	lw	sw	beq	jump
RegWrite	1	1	1	0	0	0

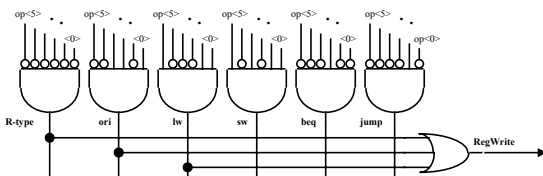- RegWrite = R-type + ori + lw
= !op<5> & !op<4> & !op<3> & !op<2> & !op<1> & !op<0> (R-type)
+ !op<5> & !op<4> & op<3> & op<2> & !op<1> & op<0> (ori)
+ op<5> & !op<4> & !op<3> & !op<2> & op<1> & op<0> (lw)



PLA Implementation of the Main Control

 

Summary

- Synchronous circuit: from clock edge to clock edge, just define what happens in between; Flip flop defined to handle conditions
- Combinational logic has no clock
- Always statements create latches if you don't specify all output for all conditions
- Verilog does not turn hardware design into writing programs; **describe** your HW design
- Control implementation: turn truth tables into logic equations