

CS152 – Computer Architecture and Engineering

Lecture 9 – Multicycle Design 2003-09-22

Dave Patterson

(www.cs.berkeley.edu/~patterson)

www-inst.eecs.berkeley.edu/~cs152/



CS 152 L09 Multicycle (1)

Patterson Fall 2003 © UCB

Review

- Synchronous circuit: from clock edge to clock edge, just define what happens in between; Flip flop defined to handle conditions
- Combinational logic has no clock
- Always statements create latches if you don't specify all output for all conditions
- Verilog does not turn hardware design into writing programs; **describe** your HW design
- Control implementation: turn truth tables into logic equations




CS 152 L09 Multicycle (2)

Patterson Fall 2003 © UCB

Recap: Processor Design is a Process

 
- Bottom-up
 - assemble components in target technology to establish critical timing
- Top-down
 - specify component behavior from high-level requirements
- Iterative refinement
 - establish partial solution, expand and improve



CS 152 L09 Multicycle (3)

Patterson Fall 2003 © UCB

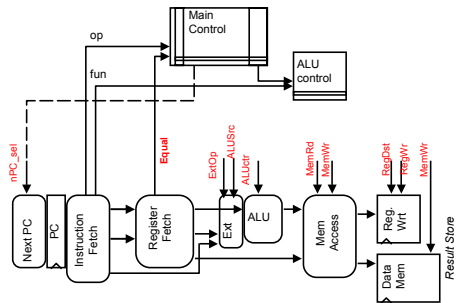Abstract View of our single cycle processor



- looks like a FSM with PC as state



CS 152 L09 Multicycle (4)

Patterson Fall 2003 © UCB

What's wrong with our CPI=1 processor?


Arithmetic & Logical



Load



Store

 

Branch



- Long Cycle Time
- All instructions take as much time as the slowest
- Real memory is not as nice as our idealized memory
 - cannot always get the job done in one (short) cycle




CS 152 L09 Multicycle (5)


Patterson Fall 2003 © UCB

Memory Access Time

 - Physics => fast memories are small (large memories are slow)



- => Use a hierarchy of memories

 


CS 152 L09 Multicycle (6)

Patterson Fall 2003 © UCB

Reducing Cycle Time

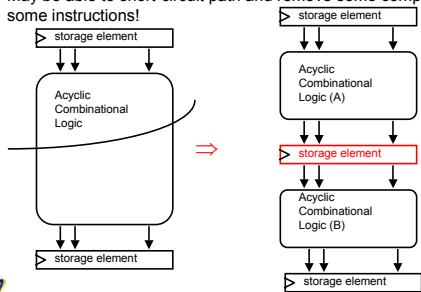
- Cut combinational dependency graph and insert register / latch
- Do same work in two fast cycles, rather than one slow one
- May be able to short-circuit path and remove some components for some instructions!



CS 162 L09 Multicycle (7)


Patterson Fall 2003 © UCB

Worst Case Timing (Load)

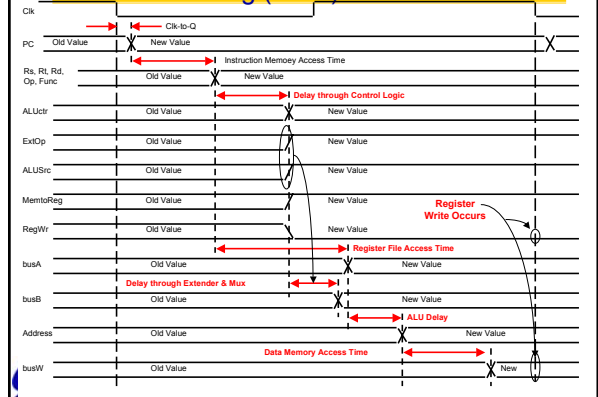

Basic Limits on Cycle Time

 - Next address logic
 - $PC \leftarrow \text{branch} ? PC + \text{offset} : PC + 4$
- Instruction Fetch
 - $\text{InstructionReg} \leftarrow \text{Mem}[PC]$
- Register Access
 - $A \leftarrow R[rs]$
- ALU operation
 - $R \leftarrow A + B$




CS 162 L09 Multicycle (9)

Patterson Fall 2003 © UCB

Partitioning the CPI=1 Datapath

- Add registers between smallest steps

 


- Place enables on all registers

Cal

CS 162 L09 Multicycle (10)

Patterson Fall 2003 © UCB

Example Multicycle Datapath

 

- Critical Path ?

Cal

CS 162 L09 Multicycle (11)

Patterson Fall 2003 © UCB

Administrivia

- Office hours in Lab
 - Mon 4 – 5:30 Jack, Tue 3:30-5 Kurt,
 - Wed 3 – 4:30 John, Thu 3:30-5 Ben
- Dave's office hours Tue 3:30 – 5
- Lab 3 demo Friday, due Monday
- Midterm I Wednesday Oct 8 5:30 - 8:30pm

Cal

CS 162 L09 Multicycle (12)

Patterson Fall 2003 © UCB

Recall: Step-by-step Processor Design

Step 1: ISA => Logical Register Transfers

Step 2: Components of the Datapath

Step 3: RTL + Components => Datapath

Step 4: Datapath + Logical RTs => Physical RTs

Step 5: Physical RTs => Control


Step 4: R-type (add, sub, ...)

- Logical Register Transfer

```
inst    Logical Register Transfers
ADDU    R[rd] <- R[rs] + R[rt]; PC <- PC + 4
```

- Physical Register Transfers
 
```
inst    Physical Register Transfers
IR <- MEM[pc]
ADDU    A <- R[rs]; B <- R[rt]
        S <- A + B
        R[rd] <- S;      PC <- PC + 4
```



CS 162 L09 Multicycle (14)

Patterson Fall 2003 © UCB


Step 4: Logical immed

- Logical Register Transfer

```
inst    Logical Register Transfers
ORI     R[rt] <- R[rs] OR ZExt(lm16); PC <- PC + 4
```

- Physical Register Transfers
 
```
inst    Physical Register Transfers
IR <- MEM[pc]
ORI     A <- R[rs]; B <- R[rt]
        S <- A OR ZExt(lm16)
        R[rt] <- S;      PC <- PC + 4
```



CS 162 L09 Multicycle (15)

Patterson Fall 2003 © UCB


Step 4 : Load

- Logical Register Transfer

```
inst    Logical Register Transfers
LW      R[rt] <- MEM[R[rs] + SExt(lm16)];
        PC <- PC + 4
```

- Physical Register Transfers
 
```
inst    Physical Register Transfers
IR <- MEM[pc]
LW      A <- R[rs]; B <- R[rt]
        S <- A + SExt(lm16)
        M <- MEM[S]
        R[rd] <- M;      PC <- PC + 4
```



CS 162 L09 Multicycle (16)

Patterson Fall 2003 © UCB


Step 4 : Store

- Logical Register Transfer

```
inst    Logical Register Transfers
SW      MEM[R[rs] + SExt(lm16)] <- R[rt];
        PC <- PC + 4
```

- Physical Register Transfers
 
```
inst    Physical Register Transfers
IR <- MEM[pc]
SW      A <- R[rs]; B <- R[rt]
        S <- A + SExt(lm16);
        MEM[S] <- B;      PC <- PC + 4
```



CS 162 L09 Multicycle (17)

Patterson Fall 2003 © UCB


Step 4 : Branch

- Logical Register Transfer

```
inst    Logical Register Transfers
BEQ     if (R[rs] == R[rt])
        then PC <- PC + 4 + SExt(lm16) || 00
        else PC <- PC + 4
```

- Physical Register Transfers
 
```
inst    Physical Register Transfers
IR <- MEM[pc]
BEQ     E <- (R[rs] == R[rt])
        if (IE) PC <- PC + 4;
        else   PC <- PC + 4 + (SExt(lm16), 2b0)
```




CS 162 L09 Multicycle (18)

Patterson Fall 2003 © UCB


Alternative datapath (book): Multiple Cycle Datapath

- Minimizes Hardware: 1 memory, 1 adder

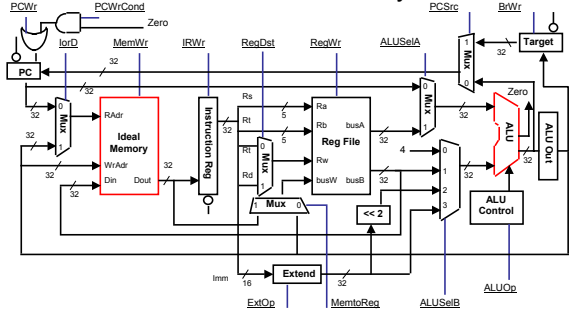


Our Control Model

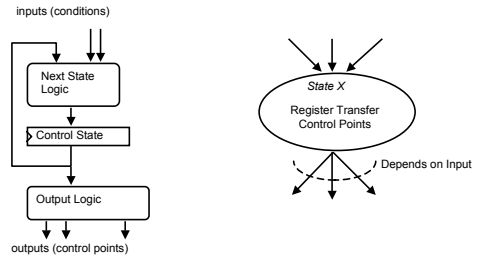- State specifies control points for Register Transfer
- Transfer occurs upon exiting state (same clock edge)



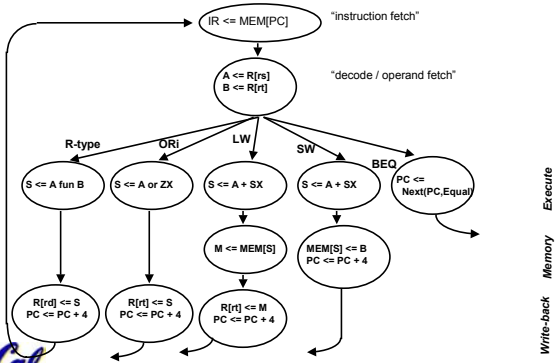
Step 4 ⇒ Control Spec for multicycle proc



Traditional FSM Controller

state	op	cond	next state	control points


Truth Table

 


Step 5 ⇒ (datapath + state diagram ⇒ control)

- Translate RTs into control points
- Assign states
- Then go build the controller

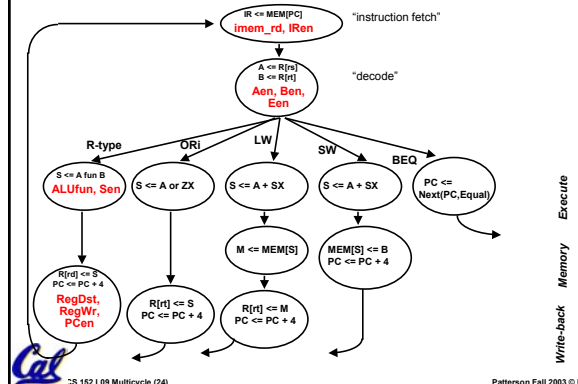Mapping Register Transfers to Control Points



Assigning States

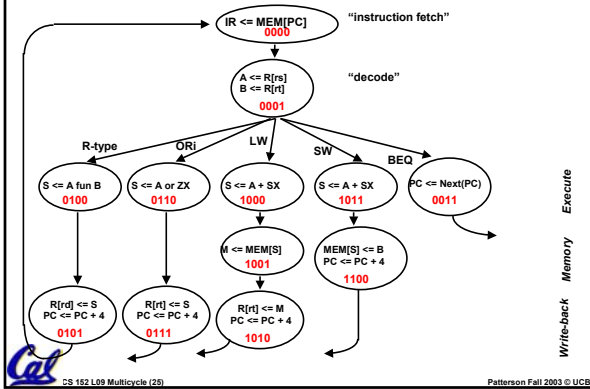

(Mostly) Detailed Control Specs (missing=>0)

State	Op field	Eq	Next IR	PC en sel	Ops A B E	Exec Ex Sr ALU S	Mem R W M	Write-Back M-R Wr Dst
0000	???????		0001	1				
0001	BEQ	x	0011		1 1 1			
0001	R-type	x	0100		1 1 1			
0001	ORI	x	0110		1 1 1			
0001	LW	x	1000		1 1 1			
0001	SW	x	1011		1 1 1			
-all same in Moore machine								
0011	BEQ	xxxxxx	0	0000	1 0			x 0 x
0011		xxxxxx	1	0000	1 1			x 0 x
0100		xxxxxx	x	0101		0 1 fun 1		
0101		xxxxxx	x	0000	1 0			0 1 1
0110		xxxxxx	x	0111		0 0 or 1		
0111		xxxxxx	x	0000	1 0			0 1 0
1000		xxxxxx	x	1001		1 0 add 1		
1001		xxxxxx	x	1010			1 0 1	
1010		xxxxxx	x	0000	1 0			1 1 0
1011		xxxxxx	x	1100		1 0 add 1		
1100		xxxxxx	x	0000	1 0		0 1 0	


Performance Evaluation

- What is the average CPI?
 - state diagram gives CPI for each instruction type
 - workload gives frequency of each type


Type	CPI, for type	Frequency	CPI, x freq,
Arith/Logic	4	40%	1.6
Load	5	30%	1.5
Store	4	10%	0.4
branch	3	20%	0.6
Average CPI:			4.1

Controller Design

 
- The state diagrams that arise define the controller for an instruction set processor are highly structured
 - Use this structure to construct a simple "microsequencer"
 - Control reduces to programming this very simple device
- => microprogramming




Example: Jump-Counter

 

Using a Jump Counter

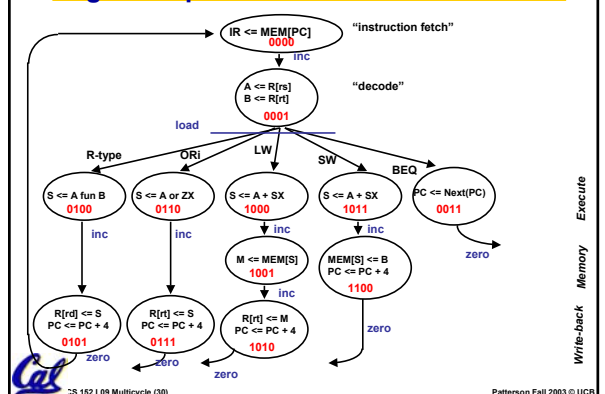

Our Microsequencer

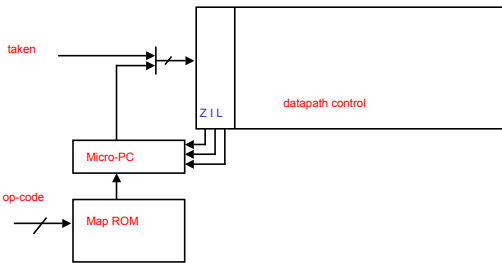

Microprogram Control Specification

μPC	Taken	Next	IR	PC	Ops en sel	Exec A B	Mem Ex Sr ALU S	Write-Back R W M	M-R Wr Dst
0000	?	inc	1						
0001	0	load			1 1				
BEQ:									
0011	0	zero			1 0				
0011	1	zero			1 1				
R:									
0100	x	inc					0 1 fun 1		0 1 1
0101	x	zero			1 0				
ORI:									
0110	x	inc					0 0 or 1		0 1 0
0111	x	zero			1 0				
LW:									
1000	x	inc					1 0 add 1	1 0 1	
1001	x	inc							
1010	x	zero			1 0				1 1 0
SW:									
1011	x	inc					1 0 add 1		
1100	x	zero			1 0			0 1 0	

Adding the Dispatch ROM


- Sequencer-based control
 - Called "microPC" or "μPC" vs. state register

Control Value Effect


- 00 Next μaddress = 0
- 01 Next μaddress = dispatch ROM
- 10 Next μaddress = μaddress + 1

ROM:


R-type	000000	0100
BEQ	000100	0011
ori	001101	0110
LW	100011	1000
SW	101011	1011

 


Example: Controlling Memory

 

Controller handles non-ideal memory

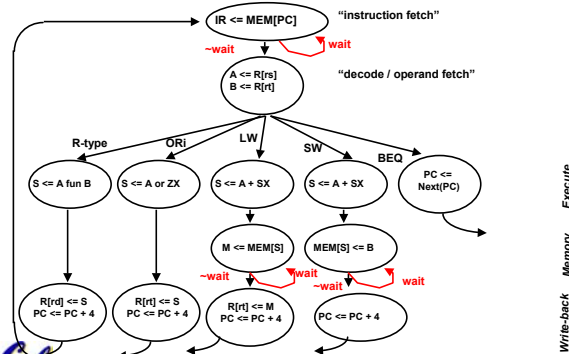

Microprogramming

 


- Microprogramming is a fundamental concept
 - implement an instruction set by building a very simple processor and interpreting the instructions
 - essential for very complex instructions and when few register transfers are possible
 - overkill when ISA matches datapath 1-1

Microprogramming

- Microprogramming is a convenient method for implementing *structured* control state diagrams:
 - Random logic replaced by microPC sequencer and ROM
 - Each line of ROM called a μ instruction: contains sequencer control + values for control points
 - limited state transitions:
 - branch to zero, next sequential,
 - branch to μ instruction address from dispatch ROM
- Horizontal μ Code: one control bit in μ Instruction for every control line in datapath
- Vertical μ Code: groups of control-lines coded together in μ Instruction (e.g. possible ALU dest)
- Control design reduces to Microprogramming
 - Part of the design process is to develop a "language" that describes control and is easy for humans to understand

"Macroinstruction" Interpretation

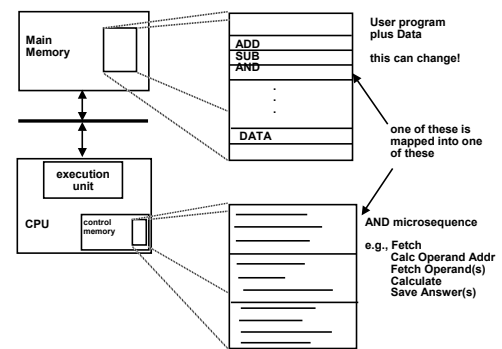


Designing a Microinstruction Set

- Start with list of control signals
 - Group signals together that make sense (vs. random): called "fields"
 - Place fields in some logical order (e.g., ALU operation & ALU operands first and microinstruction sequencing last)
 - To minimize the width, encode operations that will never be used at the same time
 - Create a symbolic legend for the microinstruction format, showing name of field values and how they set the control signals
- Use computers to design computers

Again: Alternative multicycle datapath (book)

- Mimimizes Hardware: 1 memory, 1 adder

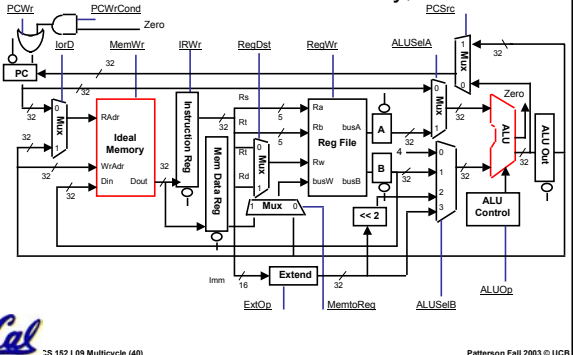

1&2) Start with list of control signals, grouped into fields

Signal name	Effect when deasserted	Effect when asserted
ALUSelA	1st ALU operand = PC	1st ALU operand = Reg[rs]
RegWrite	None	Reg. is written
MemtoReg	Reg. write data input = ALU	Reg. write data input = memory
RegDst	Reg. dest. no. = rt	Reg. dest. no. = rd
MemRead	None	Memory at address is read.
		MDR <= Mem[addr]
MemWrite	None	Memory at address is written
lorD	Memory address = PC	Memory address = S
IRWrite	None	IR <= Memory
PCWrite	None	PC <= PCSource
PCWriteCond	None	IF ALUzero then PC <= PCSource
PCSource	PCSource = ALU	PCSource = ALUout
ExtOp	Zero Extended	Sign Extended

Signal name	Value	Effect
ALUOp	00	ALU adds
	01	ALU subtracts
	10	ALU does function code
	11	ALU does logical OR
ALUSelB	00	2nd ALU input = 4
	01	2nd ALU input = Reg[rt]
	10	2nd ALU input = extended, shift left 2
	11	2nd ALU input = extended

3&4) Microinstruction Format: unencoded vs. encoded fields

Field Name	Width	Control Signals Set
wide narrow		
ALU Control	4 2	ALUOp
SRC1	2 1	ALUSelA
SRC2	5 3	ALUSelB, ExtOp
ALU Destination	3 2	RegWrite, MemtoReg, RegDst
Memory	3 2	MemRead, MemWrite, lorD
Memory Register	1 1	IRWrite
PCWrite Control	3 2	PCWrite, PCWriteCond, PCSource
Sequencing	3 2	AddrCtl
Total width	24 15	bits

5) Legend of Fields and Symbolic Names

Field Name	Values for Field	Function of Field with Specific Value
ALU	Add	ALU adds
	Subt.	ALU subtracts
	Func code	ALU does function code
SRC1	Or	ALU does logical OR
	PC	1st ALU input = PC
SRC2	rs	1st ALU input = Reg[rs]
	4	2nd ALU input = 4
	Extend0	2nd ALU input = sign ext. IR[15-0]
	Extend0	2nd ALU input = zero ext. IR[15-0]
destination	Extshft	2nd ALU input = sign ex., sl IR[15-0]
	rt	2nd ALU input = Reg[rt]
	rd ALU	Reg[rd] = ALUout
	rt ALU	Reg[rt] = ALUout
Memory	rt Mem	Reg[rt] = Mem
	Read PC	Read memory using PC
	Read ALU	Read memory using ALUout for addr
	Write ALU	Write memory using ALUout for addr
Memory register	IR	IR = Mem
	ALU	PC = ALU
PC write	ALUoutCond	IF ALU Zero then PC = ALUout
	Seq	Go to sequential μinstruction
	Fetch	Go to the first microinstruction
Sequencing	Fetch	Go to the first microinstruction
	Dispatch	Dispatch using ROM.

Quick check: what do these fieldnames mean?

Destination:

Code	Name	RegWrite	MemToReg	RegDest
00	---	0	X	X
01	rd ALU	1	0	1
10	rt ALU	1	0	0
11	rt MEM	1	1	0

SRC2:


Code	Name	ALUSelB	ExtOp
000	---	X	X
001	4	00	X
010	rt	01	X
011	ExtShft	10	1
100	Extend	11	1
111	Extend0	11	0

Specific Sequencer from before

Sequencer-based control unit from last lecture

– Called “microPC” or “μPC” vs. state register

Code	Name	Effect
00	fetch	Next μaddress = 0
01	dispatch	Next μaddress = dispatch ROM
10	seq	Next μaddress = μaddress + 1

 

Legacy Software and Microprogramming

- IBM bet company on 360 Instruction Set Architecture (ISA): single instruction set for many classes of machines
 - (8-bit to 64-bit)
- Stewart Tucker stuck with job of what to do about software compatibility
 - If microprogramming could easily do same instruction set on many different microarchitectures, then why couldn't multiple microprograms do multiple instruction sets on the same microarchitecture?
 - Coined term “emulation”: instruction set interpreter in microcode for non-native instruction set
 - Very successful: in early years of IBM 360 it was hard to know whether old instruction set or new instruction set was more frequently used

Microprogramming Pros and Cons


- Ease of design
- Flexibility
 - Easy to adapt to changes in organization, timing, technology
 - Can make changes late in design cycle, or even in the field
- Can implement very powerful instruction sets (just more control memory)
- Generality
 - Can implement multiple instruction sets on same machine.
 - Can tailor instruction set to application.
- Compatibility
 - Many organizations, same instruction set
- Costly to implement
- Slow

Thought: Microprogramming one inspiration for RISC

- If simple instruction could execute at very high clock rate...
- If you could even write compilers to produce microinstructions...
- If most programs use simple instructions and addressing modes...
- If microcode is kept in RAM instead of ROM so as to fix bugs ...
- If same memory used for control memory could be used instead as cache for “macroinstructions”...
- Then why not skip instruction interpretation by a microprogram and simply compile directly into lowest language of machine? (microprogramming is overkill when ISA matches datapath 1-1)

Overview of Control

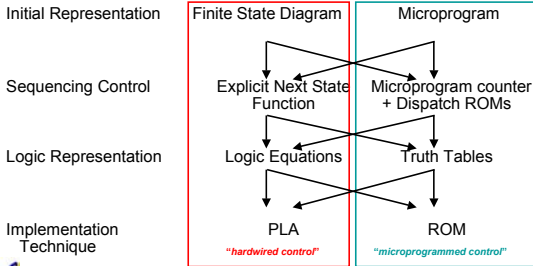- Control may be designed using one of several initial representations. The choice of sequence control, and how logic is represented, can then be determined independently; the control can then be implemented with one of several methods using a structured logic technique.



Summary (1 of 3)

- Disadvantages of the Single Cycle Processor
 - Long cycle time
 - Cycle time is too long for all instructions except the Load
- Multiple Cycle Processor:
 - Divide the instructions into smaller steps
 - Execute each step (instead of the entire instruction) in one cycle
- Partition datapath into equal size chunks to minimize cycle time
 - ~10 levels of logic between latches
- Follow same 5-step method for designing "real" processor

Summary (cont'd) (2 of 3)

- Control is specified by finite state diagram
- Specialize state-diagrams easily captured by microsequencer
 - simple increment & "branch" fields
 - datapath control fields
- Control design reduces to Microprogramming
- Control is more complicated with:
 - complex instruction sets
 - restricted datapaths (see the book)
- Simple Instruction set and powerful datapath \Rightarrow simple control
 - could try to reduce hardware (see the book)
 - rather go for speed \Rightarrow many instructions at once!

Summary (3 of 3)

- Microprogramming is a fundamental concept
 - implement an instruction set by building a very simple processor and interpreting the instructions
 - essential for very complex instructions and when few register transfers are possible
 - Control design reduces to Microprogramming*
- Design of a Microprogramming language
 - Start with list of control signals
 - Group signals together that make sense (vs. random): called "fields"
 - Place fields in some logical order (e.g., ALU operation & ALU operands first and microinstruction sequencing last)
 - To minimize the width, encode operations that will never be used at the same time
 - Create a symbolic legend for the microinstruction format, showing name of field values and how they set the control signals

Where to get more information?

- Multiple Cycle Controller: Appendix C of your text book.
- Microprogramming: Section 5.7 of your text book.
- D. Patterson, "Microprogramming," Scientific American, March 1983.
- D. Patterson and D. Ditzel, "The Case for the Reduced Instruction Set Computer," Computer Architecture News 8, 6 (October 15, 1980)

Microprogram it yourself!

Label	ALU	SRC1	SRC2	Dest.	Memory	Mem.	Reg.	PC	Write
<u>Sequencing</u>									
Fetch: Add	PC	4			Read PC	IR	ALU		Seq