

CS61C : Machine Structures

Lecture 4.1.1

Logic Gates and Combinational Logic

2004-07-12

Kurt Meinz


inst.eecs.berkeley.edu/~cs61c



CS 61C L4.1.1 Combinational Logic (1)

K. Meinz, Summer 2004 © UCB

What are "Machine Structures"?

 

Coordination of many **levels of abstraction**

We'll investigate lower abstraction layers!
(contract between HW & SW)



CS 61C L4.1.1 Combinational Logic (2)

K. Meinz, Summer 2004 © UCB

Below the Program

• High-level language program (in C)

```
swap int v[], int k){
    int temp;
    temp = v[k];
    v[k] = v[k+1];
    v[k+1] = temp;
}
```

• Assembly language program (for MIPS)

```
swap: sll    $2, $5, 2
      add    $2, $4, $2
      lw     $15, 0($2)
      lw     $16, 4($2)
      sw     $16, 0($2)
      sw     $15, 4($2)
      jr     $31
```

• Machine (object) code (for MIPS)


```
000000 000000 00101 0001000001000000
000000 00100 00010 0001000000100000 . . .
```



CS 61C L4.1.1 Combinational Logic (3)

K. Meinz, Summer 2004 © UCB

Physical Hardware - PowerPC 750

 

CS 61C L4.1.1 Combinational Logic (4)

K. Meinz, Summer 2004 © UCB

Digital Design Basics (1/2)

- Next 4 weeks: we'll study how a modern processor is built starting with basic logic elements as building blocks.

• Why study logic design?

- Understand what processors can do fast and what they can't do fast (avoid slow things if you want your code to run fast!)
- Background for more detailed hardware courses (CS 150, CS 152)



CS 61C L4.1.1 Combinational Logic (5)

K. Meinz, Summer 2004 © UCB

Digital Design Basics (2/2)

- ISA is very important abstraction layer
 - Contract between HW and SW
 - Can you peek across abstraction?
 - Can you depend "across abstraction"?
- Voltages are analog, quantized to 0/1
- Circuit delays are fact of life
- Two types
 - Stateless Combinational Logic (&, |, ~)
 - State circuits (e.g., registers)



CS 61C L4.1.1 Combinational Logic (6)

K. Meinz, Summer 2004 © UCB

Outline


- Transistors
- Logic Gates
- Combinational Logic
- Boolean Algebra



CS 61C L4.1.1 Combinational Logic (7)

K. Meitz, Summer 2004 © UCB

Transistors (1/3)

 

CMOSFET Transistors:


- * Physically exist!
- * Voltages are quantized
- * Only 2 Types:
 - P-channel: 0 on gate → pull up (1)
 - N-channel: 1 on gate → pull down (0)
- * Undriven otherwise.



CS 61C L4.1.1 Combinational Logic (8)

K. Meitz, Summer 2004 © UCB

Transistors (2/3)

 

CMOSFET Transistors:


- * have delay and require power
- * can be combined to perform logical operations and maintain state.
- logical operations will be our starting point for digital design
- state tomorrow



CS 61C L4.1.1 Combinational Logic (9)

K. Meitz, Summer 2004 © UCB

Transistors (3/3): CMOS → Nand

 

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0



CS 61C L4.1.1 Combinational Logic (10)

K. Meitz, Summer 2004 © UCB

Logic Gates (1/4)


- Transistors are too low level
 - Good for measuring performance, power.
 - Bad for logical design / analysis
- Gates are collections of transistors wired in a certain way
 - Can represent and reason about gates with truth tables and Boolean algebra
 - Assume know truth tables and Boolean algebra from a math or circuits course.
 - Section B.2 in the textbook has a review



CS 61C L4.1.1 Combinational Logic (11)


K. Meitz, Summer 2004 © UCB

Logic Gates (2/4)

 


AND

ab	c
00	0
01	0
10	0
11	1

 

OR

ab	c
00	0
01	1
10	1
11	1

 

NOT

a	b
0	1
1	0




CS 61C L4.1.1 Combinational Logic (12)

K. Meitz, Summer 2004 © UCB

Logic Gates (3/4)

AND Gate

 

Definition


A	B	C
0	0	0
0	1	0
1	0	0
1	1	1




CS 61C L4.1.1 Combinational Logic (3)

K. Meitz, Summer 2004 © UCB


Logic Gates (4/4)

 

ab	c
00	0
01	1
10	1
11	0

 

ab	c
00	1
01	1
10	1
11	0

 


ab	c
00	1
01	0
10	0
11	0



CS 61C L4.1.1 Combinational Logic (4)

K. Meitz, Summer 2004 © UCB

Truth Tables (1/6)

 

a	b	c	d	y
0	0	0	0	F(0,0,0,0)
0	0	0	1	F(0,0,0,1)
0	0	1	0	F(0,0,1,0)
0	0	1	1	F(0,0,1,1)
0	1	0	0	F(0,1,0,0)
0	1	0	1	F(0,1,0,1)
0	1	1	0	F(0,1,1,0)
0	1	1	1	F(0,1,1,1)
1	0	0	0	F(1,0,0,0)
1	0	0	1	F(1,0,0,1)
1	0	1	0	F(1,0,1,0)
1	0	1	1	F(1,0,1,1)
1	1	0	0	F(1,1,0,0)
1	1	0	1	F(1,1,0,1)
1	1	1	0	F(1,1,1,0)
1	1	1	1	F(1,1,1,1)



CS 61C L4.1.1 Combinational Logic (5)

K. Meitz, Summer 2004 © UCB

TT (2/6) Ex #1: 1 iff one (not both) a,b=1


a	b	y
0	0	0
0	1	1
1	0	1
1	1	0



CS 61C L4.1.1 Combinational Logic (6)

K. Meitz, Summer 2004 © UCB

TT (3/6): Example #2: 2-bit adder

 

A	B	C
$a_1 a_0$	$b_1 b_0$	$c_2 c_1 c_0$
00	00	000
00	01	001
00	10	010
00	11	011
01	00	001
01	01	010
01	10	011
01	11	100
10	00	010
10	01	011
10	10	100
10	11	101
11	00	011
11	01	100
11	10	101
11	11	110



CS 61C L4.1.1 Combinational Logic (7)

K. Meitz, Summer 2004 © UCB

TT (4/6): Ex #3: 32-bit unsigned adder

A	B	C
000 ... 0	000 ... 0	000 ... 00
000 ... 0	000 ... 1	000 ... 01
.	.	.
.	.	.
.	.	.
111 ... 1	111 ... 1	111 ... 10



CS 61C L4.1.1 Combinational Logic (8)

K. Meitz, Summer 2004 © UCB

TT (5/6): Conversion: 3-input majority

a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1




CS 61C L4.1.1 Combinational Logic (A9)

K. Meitz, Summer 2004 © UCB

TT (6/6): Conversion: 3-input majority

a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

CS 61C L4.1.1 Combinational Logic (B0)

K. Meitz, Summer 2004 © UCB

Combinational Logic (1/2)

A **combinational** logic block is one in which the output is a function only of its **current input**.

- Combinational logic **cannot have memory**.
- Everything we've seen so far is CL
- CL will have delay (f(transistors))
 - More later.



CS 61C L4.1.1 Combinational Logic (C1)

K. Meitz, Summer 2004 © UCB

Representations of CL Circuits (2/2)...

- Logic Gates ✓
- Truth Tables ✓
- Boolean Algebra ???



CS 61C L4.1.1 Combinational Logic (C2)

K. Meitz, Summer 2004 © UCB

Boolean Algebra (1/7)

- George Boole, 19th Century mathematician
- Developed a mathematical system (algebra) involving logic, later known as "Boolean Algebra"
- Primitive functions: AND, OR and NOT
- The power of BA is there's a one-to-one correspondence between circuits made up of AND, OR and NOT gates and equations in BA


+ means OR, • means AND, $\bar{x}$ means NOT



CS 61C L4.1.1 Combinational Logic (C3)

K. Meitz, Summer 2004 © UCB

BA (2/7): e.g., for majority fun...

 

$$y = a \cdot b + a \cdot c + b \cdot c$$

$$y = ab + ac + bc$$



CS 61C L4.1.1 Combinational Logic (C4)

K. Meitz, Summer 2004 © UCB

BA (3/7): Laws of Boolean Algebra


$x \cdot \bar{x} = 0$	$x + \bar{x} = 1$	complementarity
$x \cdot 0 = 0$	$x + 1 = 1$	laws of 0's and 1's
$x \cdot 1 = x$	$x + 0 = x$	identities
$x \cdot x = x$	$x + x = x$	idempotent law
$x \cdot y = y \cdot x$	$x + y = y + x$	commutativity
$(xy)z = x(yz)$	$(x + y) + z = x + (y + z)$	associativity
$x(y + z) = xy + xz$	$x + yz = (x + y)(x + z)$	distribution
$xy + x = x$	$(x + y)x = x$	uniting theorem
$\overline{x \cdot y} = \bar{x} + \bar{y}$	$\overline{x + y} = \bar{x} \cdot \bar{y}$	DeMorgan's Law



CS 61C L4.1.1 Combinational Logic (26)

K. Meitz, Summer 2004 © UCB

 BA (4/7): Circuit & Algebraic Simplification



original circuit

$$y = ((ab) + a) + c$$

equation derived from original circuit

$$\begin{aligned} &= ab + a + c \\ &= a(b + 1) + c \\ &= a(1) + c \\ &= a + c \end{aligned}$$

algebraic simplification



simplified circuit



CS 61C L4.1.1 Combinational Logic (26)

K. Meitz, Summer 2004 © UCB

BA (5/7): Simplification Example

$$\begin{aligned} y &= ab + a + c \\ &= a(b + 1) + c && \text{distribution, identity} \\ &= a(1) + c && \text{law of 1's} \\ &= a + c && \text{identity} \end{aligned}$$



CS 61C L4.1.1 Combinational Logic (27)

K. Meitz, Summer 2004 © UCB

BA (6/7): Canonical forms (1/2)

abc	y
$\bar{a} \cdot \bar{b} \cdot \bar{c}$	000 1
$\bar{a} \cdot \bar{b} \cdot c$	001 1
	010 0
	011 0
$a \cdot \bar{b} \cdot \bar{c}$	100 1
	101 0
$a \cdot b \cdot \bar{c}$	110 1
	111 0

Sum-of-products
(ORs of ANDs)

$$y = \bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}c + a\bar{b}\bar{c} + ab\bar{c}$$




CS 61C L4.1.1 Combinational Logic (28)

K. Meitz, Summer 2004 © UCB

BA (7/7): Canonical forms (2/2)
 
$$\begin{aligned} y &= \bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}c + a\bar{b}\bar{c} + ab\bar{c} \\ &= \bar{a}\bar{b}(\bar{c} + c) + a\bar{b}(\bar{c} + c) && \text{distribution} \\ &= \bar{a}\bar{b}(1) + a\bar{b}(1) && \text{complementarity} \\ &= \bar{a}\bar{b} + a\bar{b} && \text{identity} \end{aligned}$$




CS 61C L4.1.1 Combinational Logic (29)

K. Meitz, Summer 2004 © UCB

"And In conclusion..."

 - Use this table and techniques we learned to transform from 1 to another



CS 61C L4.1.1 Combinational Logic (30)

K. Meitz, Summer 2004 © UCB