

CS61C : Machine Structures

Lecture 4.1.2

State and FSMs

2004-07-13

Kurt Meinz

`inst.eecs.berkeley.edu/~cs61c`




Outline

- **CL Blocks**
- **Waveforms**
- **State**
- **Clocks**
- **FSMs**




Review (1/3)

 - Use this table and techniques we learned to transform from 1 to another



 (2/3): Circuit & Algebraic Simplification




original circuit

$$y = ((ab) + a) + c$$

equation derived from original circuit

$$\begin{aligned} &\downarrow \\ &= ab + a + c \\ &\downarrow \\ &= a(b + 1) + c \\ &= a(1) + c \\ &= a + c \end{aligned}$$

algebraic simplification

 

simplified circuit

(3/3):Laws of Boolean Algebra

$$x \cdot \bar{x} = 0$$

$$x \cdot 0 = 0$$

$$x \cdot 1 = x$$

$$x \cdot x = x$$

$$x \cdot y = y \cdot x$$

$$(xy)z = x(yz)$$

$$x(y + z) = xy + xz$$

$$xy + x = x$$

$$\overline{x \cdot y} = \bar{x} + \bar{y}$$

$$x + \bar{x} = 1$$

$$x + 1 = 1$$

$$x + 0 = x$$

$$x + x = x$$

$$x + y = y + x$$

$$(x + y) + z = x + (y + z)$$

$$x + yz = (x + y)(x + z)$$

$$(x + y)x = x$$

$$\overline{(x + y)} = \bar{x} \cdot \bar{y}$$

complementarity
laws of 0's and 1's
identities
idempotent law
commutativity
associativity
distribution
uniting theorem
DeMorgan's Law




CL Blocks


- **Let's use our skills to build some CL blocks:**
 - **Multiplexer (mux)**
 - **Adder**
 - **ALU**



 Data Multiplexor (here 2-to-1, n-bit-wide)



N instances of 1-bit-wide mux

 


s	ab	c
0	00	0
0	01	0
0	10	1
0	11	1
1	00	0
1	01	1
1	10	0
1	11	1

$$\begin{aligned}c &= \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab \\&= \bar{s}(a\bar{b} + ab) + s(\bar{a}b + ab) \\&= \bar{s}(a(\bar{b} + b)) + s((\bar{a} + a)b) \\&= \bar{s}(a(1) + s((1)b) \\&= \bar{s}a + sb\end{aligned}$$




How do we build a 1-bit-wide mux?

$$\bar{s}a + sb$$

 


4-to-1 Multiplexor?

 

$$e = \overline{s_1}\overline{s_0}a + \overline{s_1}s_0b + s_1\overline{s_0}c + s_1s_0d$$

An Alternative Approach

 


Hierarchically!



Arithmetic and Logic Unit

 - Most processors contain a logic block called “Arithmetic/Logic Unit” (ALU)
- We’ll show you an easy one that does ADD, SUB, bitwise AND, bitwise OR



when $S=00$, $R=A+B$


when $S=01$, $R=A-B$

when $S=10$, $R=A \text{ AND } B$

when $S=11$, $R=A \text{ OR } B$



Our simple ALU

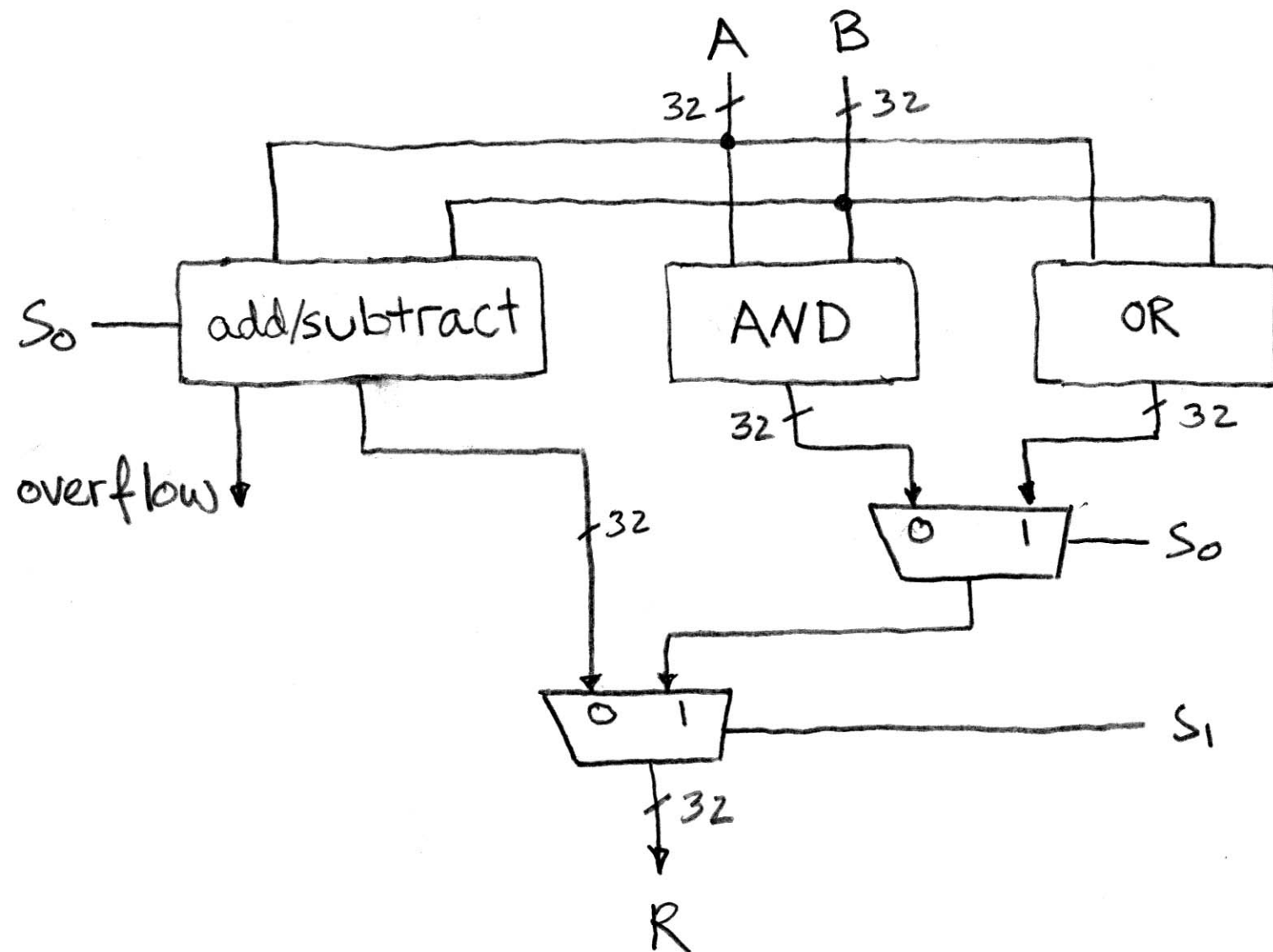


Adder/Subtractor Design -- how?

- Truth-table, then determine canonical form, then minimize and implement as we've seen before
- Look at breaking the problem down into smaller pieces that we can cascade or hierarchically layer



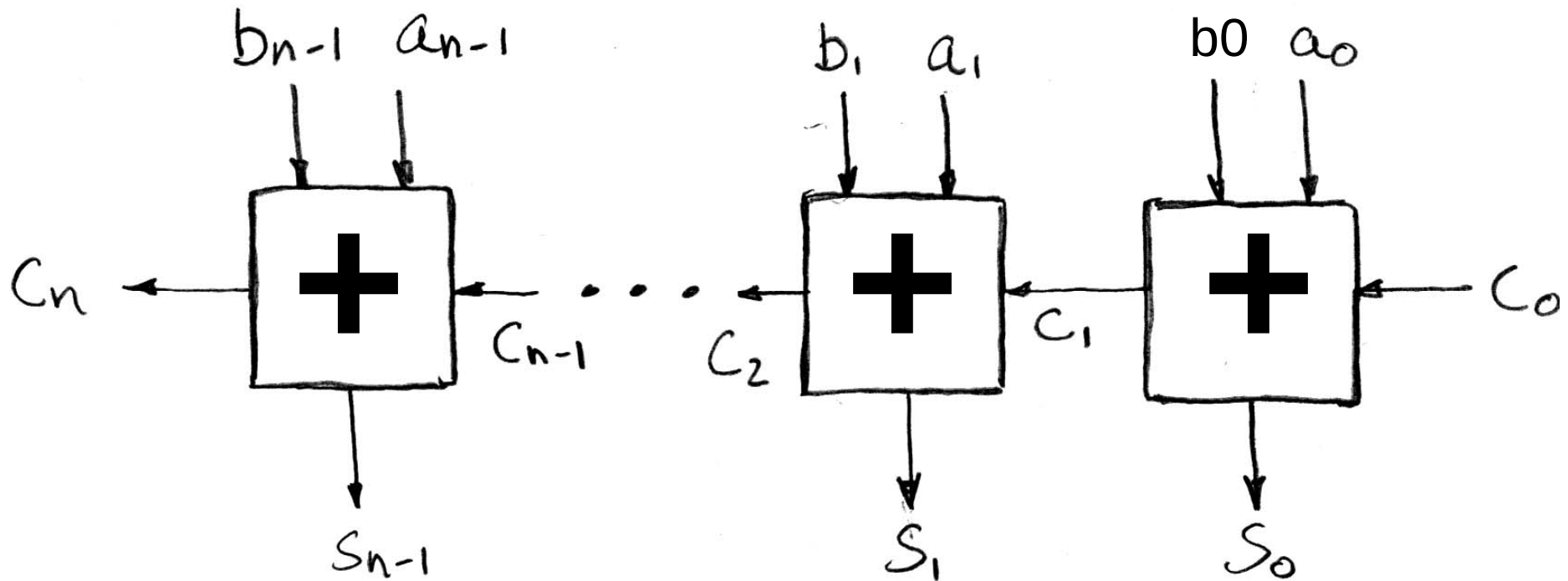N 1-bit adders $\Rightarrow$ 1 N-bit adder



Adder/Subtractor – One-bit adder LSB...

	a_3	a_2	a_1	a_0
+	b_3	b_2	b_1	b_0
	s_3	s_2	s_1	s_0

a_0	b_0	s_0	c_1
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$s_0 = a_0 \text{ XOR } b_0$$

$$c_1 = a_0 \text{ AND } b_0$$



Adder/Subtractor – One-bit adder (1/2)...

	a_3	a_2	a_1	a_0
+	b_3	b_2	b_1	b_0
	s_3	s_2	s_1	s_0



a_i	b_i	c_i	s_i	c_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$s_i = \text{XOR}(a_i, b_i, c_i)$$

$$c_{i+1} = \text{MAJ}(a_i, b_i, c_i) = a_i b_i + a_i c_i + b_i c_i$$



 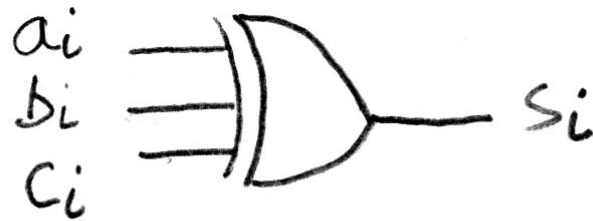
Adder/Subtractor – One-bit adder (2/2)...



$$s_i = \text{XOR}(a_i, b_i, c_i)$$

$$c_{i+1} = \text{MAJ}(a_i, b_i, c_i) = a_i b_i + a_i c_i + b_i c_i$$

Extremely Clever Subtractor


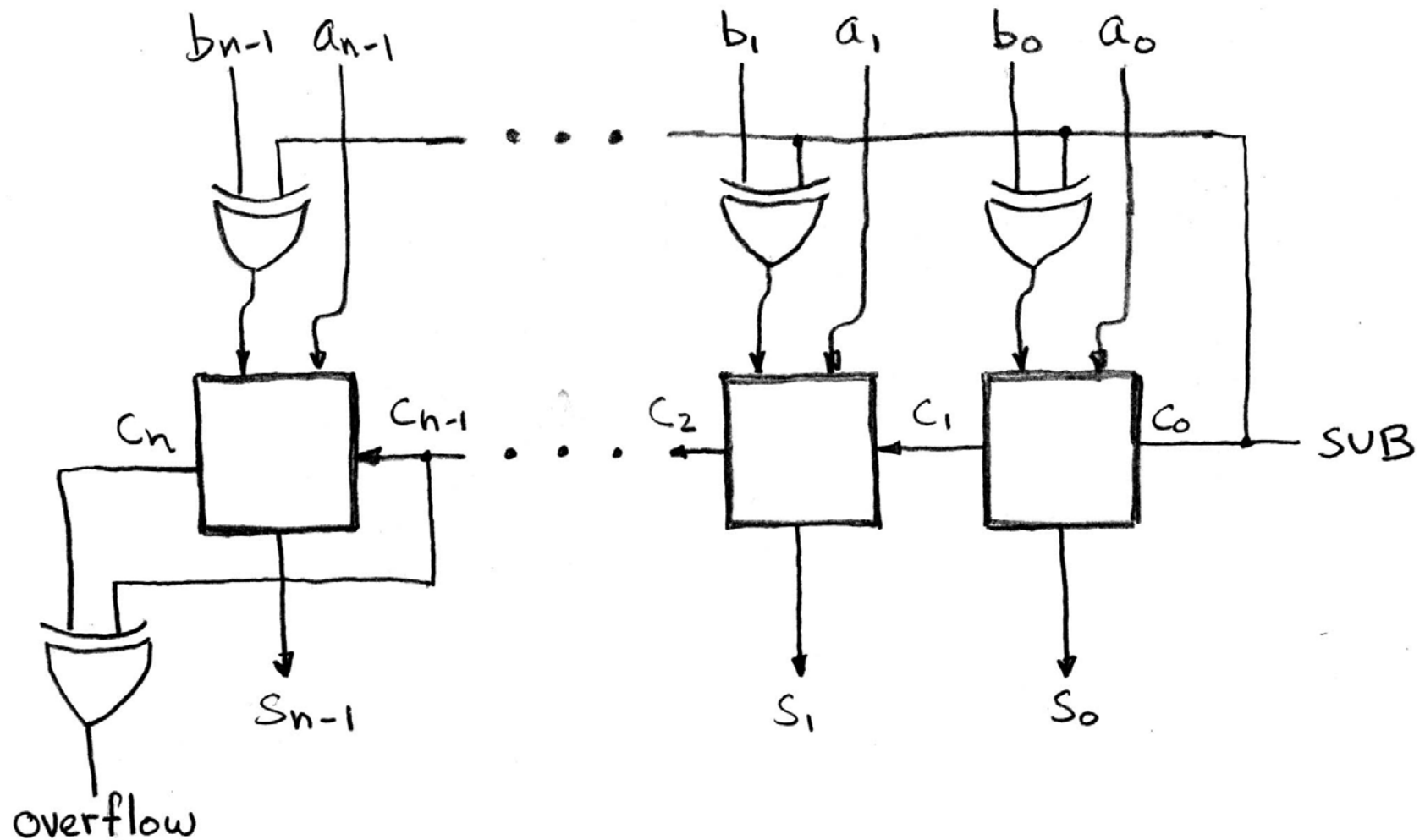


Signals and Waveforms (1/4)


- **Outputs of CL change over time**
 - **With what? → Change in inputs**
- **Can graph changes with waveforms ...**



Signals and Waveforms (2/4): Adders

  

Signals and Waveforms (3/4): Grouping


 


Signals and Waveforms (4/4): Circuit Delay



$$A = [a_3, a_2, a_1, a_0]$$

$$B = [b_3, b_2, b_1, b_0]$$

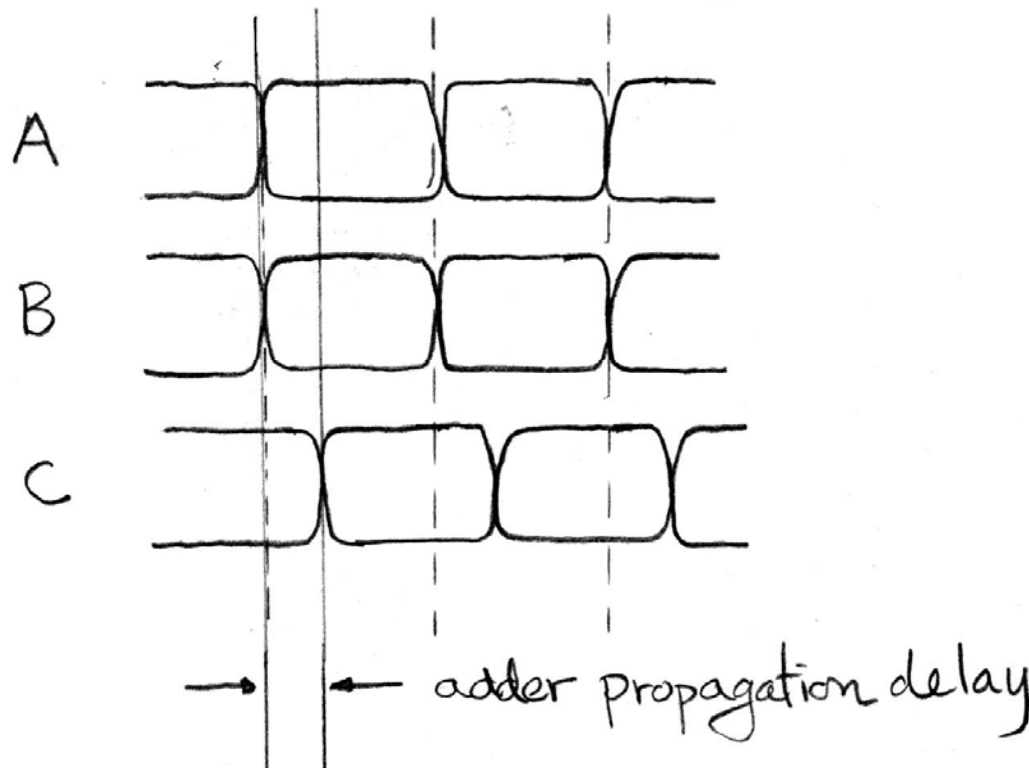 


State

- With CL, output is always a function of **CURRENT** input
 - With some (variable) propagation delay
- Clearly, we need a way to introduce state into computation




Accumulator Example

 

Want: $S=0$; for i from 0 to $n-1$
 $S = S + X_i$

First try...Does this work?

 

Nope!


Reason #1... What is there to control the next iteration of the 'for' loop?

Reason #2... How do we say: 'S=0'?



Need a way to store partial sums! ...


Circuits with STATE (e.g., register)

 


Need a Logic Block that will:

- 1. store output (partial sum) for a while,**
- 2. until we tell it to update with a new value.**


Second try...How about this? Yep!

 

Rough
timing...

 

State

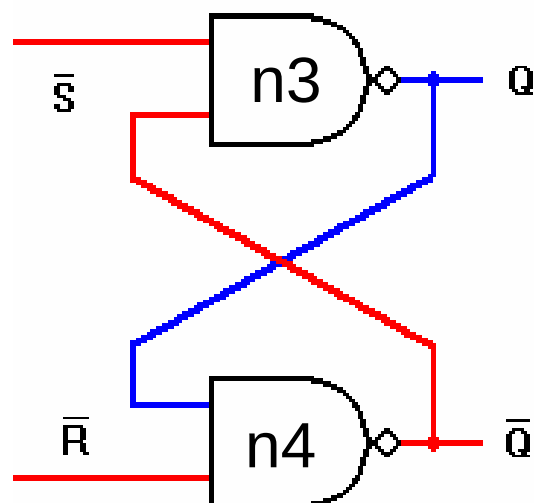


<u>A</u>	<u>B</u>	<u>O</u>
0	0	1
0	1	1
1	0	1
1	1	1

- $S=1, R=0 \rightarrow \bar{S}=0, \bar{R}=1 \rightarrow Q=1 \rightarrow \bar{Q}=0$
- $S=0, R=1 \rightarrow \bar{S}=1, \bar{R}=0 \rightarrow \bar{Q}=1 \rightarrow Q=0$
- $S=0, R=0 \rightarrow \bar{S}=1, \bar{R}=1 \rightarrow \bar{Q} \leq \text{not } Q$
 $Q \leq \text{not } \bar{Q}$




State

 


- **When CLK is low:**
 - $n1$ and $n2 = 1 \rightarrow$ no change
- **When CLK is high:**
 - $S, R = 0 \rightarrow n1, n2 = 1 \rightarrow$ no change
 - $S=1, R=0 \rightarrow n1=0, n1=1 \rightarrow Q = 1, Qbar = 0$

State

 


- This is a “rising-edge D Flip-Flop”
 - When the CLK transitions from 0 to 1 (rising edge) ...
 - $Q \leftarrow D$; $Q_{\text{bar}} \leftarrow \text{not } D$
 - All other times: $Q \leftarrow Q$; $Q_{\text{bar}} \leftarrow Q_{\text{bar}}$

D Flip Flop

 

- Called “edge-sensitive”
- RS latches: “level sensitive”


Storage Element's Timing Model

 

- **Setup Time:** Input must be stable **BEFORE** trigger clock edge
- **Hold Time:** Input must **REMAIN** stable after trigger clock edge
- **Clock-to-Q time:**
 - Output cannot change instantaneously at the trigger clock edge
 - Similar to delay in logic gates




Bus a bunch of D FFs together ...

 


- Register of size N:
 - n instances of D Flip-Flop



Second try...How about this? Yep!

 



Rough
timing...

 

  Accumulator Revisited (proper timing 1/2)



  Accumulator Revisited (proper timing 2/2)



Clocks


- Need a regular oscillator:




- Wire up three inverters in feedback?...
 - Not stable enough
 - 1- $\rightarrow$ 0 and 0- $\rightarrow$ 1 transitions not symmetric.
- Solution: Base oscillation on a natural resonance. But of what?



Clocks

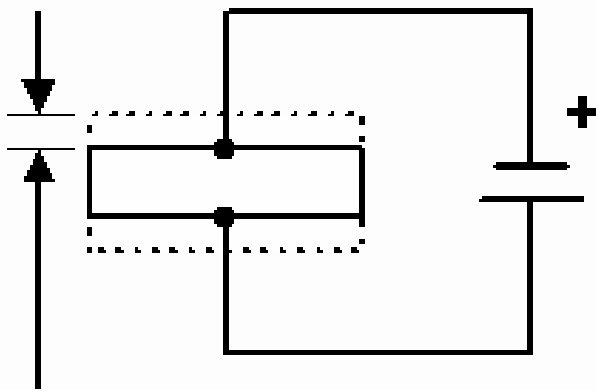

 
APPLIED VOLTAGE
CAUSES PHYSICAL
CONTRACTION



APPLIED FORCE
PRODUCES
VOLTAGE

- **Crystals and the Piezoelectric effect:**
 - Voltage $\rightarrow$ deformation $\rightarrow$ voltage $\rightarrow$...
 - Deformations have a resonant freq.
 - Function of crystal cut

Clocks

 

- **Controller puts AC across crystal:**
 - At anything but resonant freqs → destructive interference
 - Resonant freq → **CONSTRUCTIVE!**

Signals and Waveforms: Clocks

