

CS61C : Machine Structures

Lecture 5.1.1

CPU Design I

2004-07-19


Kurt Meinz

inst.eecs.berkeley.edu/~cs61c



Review: Verilog Dataflow Paradigm

```
module and_or(Z, A, B, Sel);  
    input A, B, Sel  
    output Z;  
    wire Z;  
    assign #5 Z = Sel ? (A & B) : (A | B);  
endmodule
```

 

- **Continuous Assignment:**
 - Limited to simple operations
 - Simple translation to structural
 - Trinary if (? :), logic operators
- **Excellent for CL.**




Review: What's a reg??


- Output types:
 - Structural → Wire
 - **wire** a,b,c; and (a, b, c);
 - Continuous Assign → Wire
 - **wire** a,b,c; assign a = b & c;
 - Procedural Assign → **REG**
 - wire b,c; **reg** a; always @ (b or c) a = b & c;
- Why?
 - Structural, continuous always function of current input. → simple wire
 - REG ↔ Verilog has to remember value



Anatomy: 5 components of any Computer

 

This week

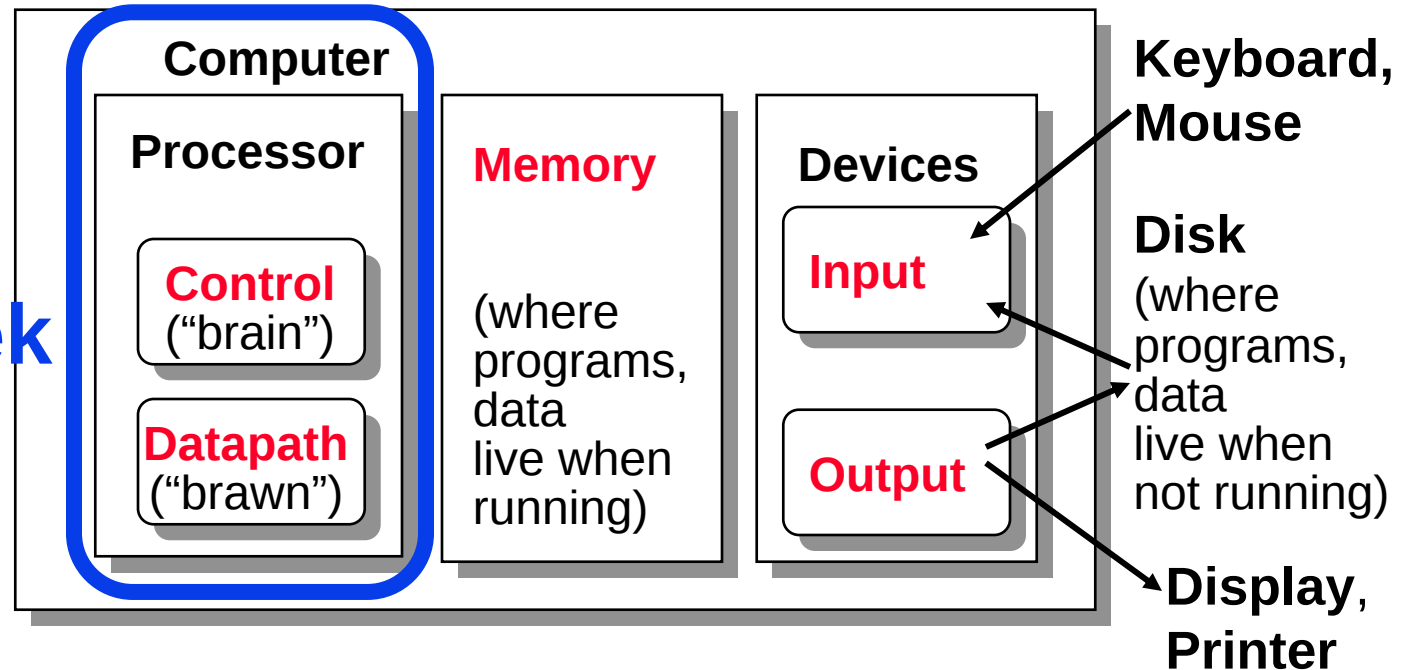

Outline

- **Design a processor: step-by-step**
- **Requirements of the Instruction Set**
- **Hardware components that match the instruction set requirements**



How to Design a Processor: step-by-step


- 1. Analyze instruction set architecture (ISA)
=> datapath requirements
 - meaning of each instruction is given by the *register transfers*
 - datapath must include storage element for ISA registers
 - datapath must support each register transfer
- 2. Select set of datapath components and establish clocking methodology
- 3. Assemble datapath meeting requirements
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- 5. Assemble the control logic




Step 1: The MIPS Instruction Formats

- All MIPS instructions are 32 bits long. 3 formats:


- R-type

 

- I-type

 

- J-type

 

- The different fields are:

- **op**: operation (“opcode”) of the instruction
- **rs, rt, rd**: the source and destination register specifiers
- **shamt**: shift amount
- **funct**: selects the variant of the operation in the “op” field
- **address / immediate**: address offset or immediate value
- **target address**: target address of jump instruction




Step 1: The MIPS-lite Subset for today

• ADD and SUB


• `addU rd,rs,rt`

• `subU rd,rs,rt`

 

• OR Immediate:


• `ori rt,rs,imm16`

 

• LOAD and STORE Word


• `lw rt,rs,imm16`

• `sw rt,rs,imm16`

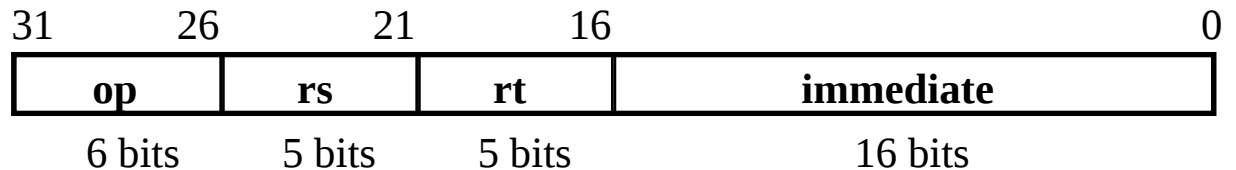

• BRANCH:

• `beq rs,rt,imm16`

 

Step 1: Register Transfer Language

- RTL gives the meaning of the instructions

{op , rs , rt , rd , shamt , funct} = MEM[PC]

{op , rs , rt , Imm16} = MEM[PC]

- All start by fetching the instruction

inst Register Transfers

ADDU **R[rd] = R[rs] + R[rt];** **PC = PC + 4**

SUBU **R[rd] = R[rs] - R[rt];** **PC = PC + 4**

ORI **R[rt] = R[rs] | zero_ext(Imm16);** **PC = PC + 4**

LOAD $R[rt] = \text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})]; PC = PC + 4$

STORE MEM[R[rs] + sign_ext(Imm16)] = R[rt]; PC = PC + 4

BEQ	if (R[rs] == R[rt]) then PC = PC + 4 + sign_ext(Imm16)] << 2 else PC = PC + 4
-----	---




Step 1: Requirements of the Instruction Set

- **Memory (MEM)**
 - instructions & data
- **Registers (R: 32 x 32)**
 - read RS
 - read RT
 - Write RT or RD
- **PC**
- **Extender (sign extend)**
- **Add and Sub register or extended immediate**
- **Add 4 or extended immediate to PC**



Step 1: Abstract Implementation

 

How to Design a Processor: step-by-step

- 1. Analyze instruction set architecture (ISA)
=> datapath requirements
 - meaning of each instruction is given by the *register transfers*
 - datapath must include storage element for ISA registers
 - datapath must support each register transfer
- 2. Select set of datapath components and establish clocking methodology
- 3. Assemble datapath meeting requirements
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- 5. Assemble the control logic (hard part!)



Step 2a: Components of the Datapath

- **Combinational Elements**
- **Storage Elements**
 - Clocking methodology



Combinational Logic: 16-bit Sign Extender

//Sign extender from 16- to 32-bits.

```
module signExtend (in,out);
```

```
    input  [15:0] in;
```

```
    output [31:0] out;
```

```
    reg    [31:0] out;
```

```
    assign
```

```
    out = { in[15], in[15], in[15], in[15],  
            in[15], in[15], in[15], in[15],  
            in[15], in[15], in[15], in[15],  
            in[15], in[15], in[15], in[15],  
            in[15:0] };
```

```
endmodule // signExtend
```



Combinational Logic: 2-bit Left Shift

```
// 32-bit Shift left by 2
module leftShift2 (in,out);
    input [31:0] in;
    output [31:0] out;


    assign
        out = { in[29:0], 1'b0, 1'b0 };
endmodule // leftShift2
```

(Also: `assign out = in[29:0] << 2;`)





Combinational Logic: More Elements

- Adder

 

- MUX

  

Combinational Logic: 32-bit Adder

```
//Behavioral model of 32-bit adder.  
module add32 (S, A, B);  
    input    [31:0] A, B;    // 32 bits  
    output   [31:0] S;  
    reg      [31:0] S;  
  
    always @ (A or B)  
        S = A + B;  
endmodule // add32
```

How do we make this dataflow?



Combinational Logic: 32-bit Mux

```
// Behavioral model of 32-bit wide
// 2-to-1 multiplexor.
module mux32 (in0,in1,select,out);
    input [31:0] in0,in1;
    input      select;
    output [31:0] out;

    reg [31:0] out;
    always @ (in0 or in1 or select)
        if (select) out=in1;
        else out=in0;

endmodule // mux32
```



CL: ALU for MIPS-lite (1/4)

- Addition, subtraction, logical OR, ==:

ADDU $R[rd] = R[rs] + R[rt]; \dots$

SUBU $R[rd] = R[rs] - R[rt]; \dots$

ORI $R[rt] = R[rs] \mid \text{zero_ext}(\text{Imm16}) \dots$

BEQ $\text{if } (R[rs] == R[rt]) \dots$

- Test to see if output == 0 for any ALU operation gives == test. How?
- P&H Section 4.5 also adds AND, Set Less Than (1 if $A < B$, 0 otherwise)
- Behavioral ALU follows sec 4.5



CL: ALU (2/4)

```
//Behavioral model of ALU:  
// 8 functions and "zero" flag,  
// A is top input, B is bottom,  
// according to P&H figure 5.19.
```

```
module ALU (A,B,control,zero,result);  
    input    [31:0] A, B;  
    input    [2:0]  control;  
    output   zero;  // used for beq,bne  
    output   [31:0] result;
```

```
    reg [31:0] result, temp;  
    always @ (A or B or control)...
```



CL: ALU (3/4)

```
reg [31:0] result, C;
always @ (A or B or control)
begin
  case (control)
    3'b000: // AND
      result=A&B;
    3'b001: // OR
      result=A|B;
    3'b010: // add
      result=A+B;
    3'b110: // subtract
      result=A-B;
    3'b111: // slt
      result=(A<B)? 1 : 0;
  endcase // case(control)
end // always @ (A or B or control)
assign zero = (result==0);
endmodule // ALU
```



☹️Unsigned compare! Can you fix it?

CL: ALU (4/4)

```
// if A and B have the same sign,  
// then A<B works (slt == 1 if A-B<0)  
// if A and B have different signs,  
// then A<B if A is negative  
// (slt == 1 if A<0)
```

```
3'b111: // slt  
    begin  
        temp = A - B;  
        result = (A[31]^B[31]) ?  
                   A[31] :  
                   temp[31];  
    end  
    . . .
```



Step 2b: Components of the Datapath

- **Combinational Elements**
- **Storage Elements**
 - Clocking methodology



Storage Element: Idealized Memory

- **Memory (idealized)**


- One input bus: Data In
- One output bus: Data Out

- **Memory word is selected by:**

- Address selects the word to put on Data Out
- Write Enable = 1: address selects the memory word to be written via the Data In bus

- **Clock input (CLK)**

 - The CLK input is a factor **ONLY** during write operation
- During read operation, behaves as a combinational logic block:
 - Address valid $\Rightarrow$ Data Out valid after “access time.”



Verilog Memory for MIPS Interpreter (1/3)

```
//Behavioral model of Random Access Memory:  
// 32-bit wide, 256 words deep,  
// asynchronous read-port if RD=1,  
// synchronous write-port if WR=1,  
// initialize from hex file ("data.dat")  
// on positive edge of reset signal,  
// dump to binary file ("dump.dat")  
// on positive edge of dump signal.
```

```
module mem  
  (CLK, RST, DMP, WR, RD, address, writeD, readD);  
  input CLK, RST, DMP, WR, RD;  
  input [31:0] address, writeD;  
  output [31:0] readD;  
  reg [31:0] readD;  
  parameter memSize=256;  
  reg [31:0] memArray [0:memSize-1];  
  integer chann, i;
```



Verilog Memory for MIPS Interpreter (2/3)

```
integer      chann, i;  
always @ (posedge RST)  
    $readmemh("data.dat", memArray);
```

```
// write if WR & positive clock edge (synchronous)  
always @ (posedge CLK)  
    if (WR) memArray[address[9:2]] =  
        writD;
```

```
// read if RD, independent of clock (asynchronous)  
always @ (address or RD) *  
    if (RD)  
        readD = memArray[address[9:2]];
```

endmodule

☹ See how sneaky sensitivity lists can be!

Use an assign!



Why is it “memArray[address[9:2]]”?

- Our memory is always byte-addressed
 - We can 1b from 0x0, 0x1, 0x2, 0x3, ...
- 1w only reads word-aligned requests
 - We only call 1w with 0x0, 0x4, 0x8, 0xC, ...
 - I.e., the last two bits are always 0
- memArray is a word wide and 2^8 deep
 - reg [31:0] memArray [0:256-1];
 - Size = 4 Bytes/row * 256 rows = 1024 B
 - If we're simulating 1w/sw, we R/W words
 - What bits select the first 256 words? [9:2]!
 - 1st word = 0x0 = 0b000 = memArray[0];
2nd word = 0x4 = 0b100 = memArray[1], etc.




Verilog Memory for MIPS Interpreter (3/3)

```
end;  
always @ (posedge DMP)  
begin  
    chann = $fopen("dump.dat");  
    if (chann==0)  
        begin  
            $display("$fopen of dump.dat  
failed.");  
            $finish;  
        end  
    // Temp variables chan, i  
    for (i=0; i<memSize; i=i+1)  
        begin  
            $fdisplay(chann, "%b",  
memArray[i]);  
        end  
    end  
end // always @ (posedge DMP)  
endmodule // mem
```



Storage Element: Register (Building Block)

- **32-bit Register**
 - **Similar to the D Flip Flop except**
 - N-bit input and output
 - Write Enable input (CE)
 - **Write Enable:**
 - negated (or deasserted) (0):
Data Out will not change
 - asserted (1):
Data Out will become Data In

 

Verilog 32-bit Register

```
// Behavioral model of 32-bit Register:  
// positive edge-triggered,  
// synchronous active-high reset.  
module reg32 (CLK, Q, D, RST);  
    input    [31:0] D;  
    input    CLK, RST;  
    output   [31:0] Q;  
  
    reg [31:0] Q;  
    always @ (posedge CLK)  
        if (RST) Q = 0; else Q = D;  
endmodule // reg32
```

