

CS61C : Machine Structures

Lecture 5.1.2

CPU Design II


2004-07-20

Kurt Meinz


inst.eecs.berkeley.edu/~cs61c




Anatomy: 5 components of any Computer

 

This week

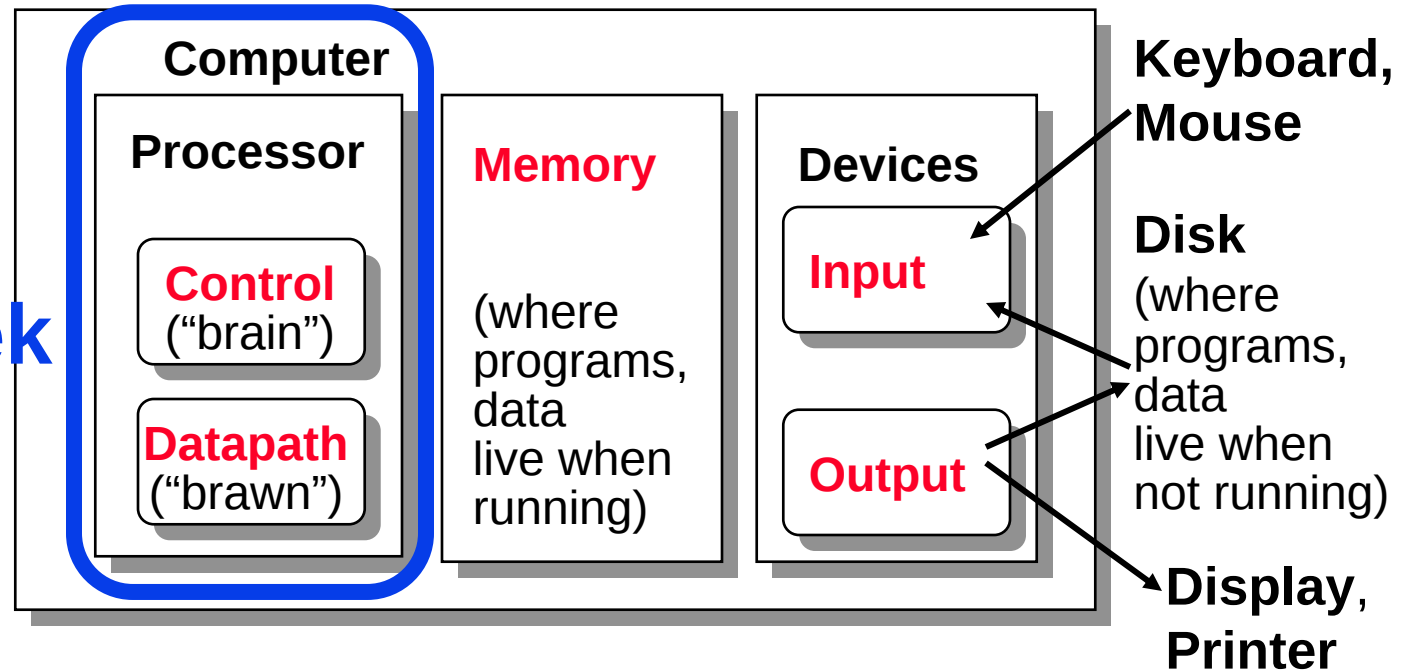

Step 1: Abstract Implementation

 


Step 2b: Components of the Datapath

- **Combinational Elements**
- **Storage Elements**
 - Clocking methodology



Storage Element: Idealized Memory

- **Memory (idealized)**
 - One input bus: Data In
 - One output bus: Data Out
- **Memory word is selected by:**
 - Address selects the word to put on Data Out
 - Write Enable = 1: address selects the memory word to be written via the Data In bus
- **Clock input (CLK)**
 - The CLK input is a factor ONLY during write operation
 - During read operation, behaves as a combinational logic block:
 - Address valid $\Rightarrow$ Data Out valid after “access time.”

 

Verilog Memory for MIPS Interpreter (1/3)

```
//Behavioral model of Random Access Memory:  
// 32-bit wide, 256 words deep,  
// asynchronous read-port if RD=1,  
// synchronous write-port if WR=1,  
// initialize from hex file ("data.dat")  
// on positive edge of reset signal,  
// dump to binary file ("dump.dat")  
// on positive edge of dump signal.
```

```
module mem  
  (CLK, RST, DMP, WR, RD, address, writeD, readD);  
  input CLK, RST, DMP, WR, RD;  
  input [31:0] address, writeD;  
  output [31:0] readD;  
  reg [31:0] readD;  
  parameter memSize=256;  
  reg [31:0] memArray [0:memSize-1];  
  integer chann, i;
```



Verilog Memory for MIPS Interpreter (2/3)

```
integer      chann, i;  
always @ (posedge RST)  
    $readmemh("data.dat", memArray);
```

```
// write if WR & positive clock edge (synchronous)  
always @ (posedge CLK)  
    if (WR) memArray[address[9:2]] =  
        writD;
```

```
// read if RD, independent of clock (asynchronous)  
always @ (address or RD) *  
    if (RD)  
        readD = memArray[address[9:2]];
```

endmodule

☹ See how sneaky sensitivity lists can be!

Use an assign!



Why is it “memArray[address[9:2]]”?

- Our memory is always byte-addressed
 - We can 1b from 0x0, 0x1, 0x2, 0x3, ...
- 1w only reads word-aligned requests
 - We only call 1w with 0x0, 0x4, 0x8, 0xC, ...
 - I.e., the last two bits are always 0
- memArray is a word wide and 2^8 deep
 - reg [31:0] memArray [0:256-1];
 - Size = 4 Bytes/row * 256 rows = 1024 B
 - If we're simulating 1w/sw, we R/W words
 - What bits select the first 256 words? [9:2]!
 - 1st word = 0x0 = 0b000 = memArray[0];
2nd word = 0x4 = 0b100 = memArray[1], etc.




Verilog Memory for MIPS Interpreter (3/3)

```
end;  
always @ (posedge DMP)  
begin  
    chann = $fopen("dump.dat");  
    if (chann==0)  
        begin  
            $display("$fopen of dump.dat  
failed.");  
            $finish;  
        end  
        // Temp variables chan, i  
        for (i=0; i<memSize; i=i+1)  
            begin  
                $fdisplay(chann, "%b",  
                           memArray[i]);  
            end  
        end  
end // always @ (posedge DMP)  
endmodule // mem
```



Storage Element: Register (Building Block)

- **32-bit Register**
 - **Similar to the D Flip Flop except**
 - N-bit input and output
 - Write Enable input (CE)
 - **Write Enable:**
 - negated (or deasserted) (0):
Data Out will not change
 - asserted (1):
Data Out will become Data In

 

Verilog 32-bit Register


```
// Behavioral model of 32-bit Register:  
// positive edge-triggered,  
// synchronous active-high reset.  
module reg32 (CLK, Q, D, RST);  
    input    [31:0] D;  
    input    CLK, RST;  
    output   [31:0] Q;  
  
    reg [31:0] Q;  
    always @ (posedge CLK)  
        if (RST) Q = 0; else Q = D;  
endmodule // reg32
```



Storage Element: Register File

- Register File consists of 32 registers:

 - Two 32-bit output busses:
busA and busB
- One 32-bit input bus: busW



- Register is selected by:

- RA (number) selects the register to put on busA (data)
- RB (number) selects the register to put on busB (data)
- RW (number) selects the register to be written via busW (data) when Write Enable is 1

- Clock input (CLK)

- The CLK input is a factor ONLY during write operation
- During read operation, behaves as a combinational logic block:

- RA or RB valid => busA or busB valid after “access time.”



Verilog Register File (1/4)

```
// Behavioral model of register file:  
// 32-bit wide, 32 words deep,  
// two asynchronous read-ports,  
// one synchronous write-port.  
// Dump register file contents to  
// console on pos edge of dump signal.
```



Verilog Register File (2/4)

```
module regFile (CLK, wEnb, DMP,  
    writeReg, writeD, readReg1, readD1,  
    readReg2, readD2);  
    input CLK, wEnb, DMP;  
    input [4:0] writeReg, readReg1,  
                readReg2;  
    input [31:0] writeD;  
    output [31:0] readD1, readD2;  
    reg [31:0] readD1, readD2;  
    reg [31:0] array [0:31];  
    reg dirty1, dirty2;  
    integer    i;
```

- 3 5-bit fields to select registers: 1 write register, 2 read register



Verilog Register File (3/4)

```
always @ (posedge CLK)
    if (wEnb)
        if (writeReg!=5'h0) // why?
            begin
                array[writeReg] = writeD;
                dirty1=1'b1; //why?
                dirty2=1'b1;
            end
always @ (readReg1 or dirty1)
    begin
        readD1 = array[readReg1];
        dirty1=0;
    end
end
```



Verilog Register File (4/4)

Problem 1: dirty1 is awful!!

```
assign readD2 = array[readReg2];
```

Problem 2:

Synchronous reads?

- must happen on posedge
- must get new value if written

```
always @ (posedge clock)
  if (readReg2 == writeReg)
    readD2 = writeD; //"forwarding"!
  else
    readD2 = array[readReg2];
```



How to Design a Processor: step-by-step

- 1. Analyze instruction set architecture (ISA)
=> datapath requirements
 - meaning of each instruction is given by the *register transfers*
 - datapath must include storage element for ISA registers
 - datapath must support each register transfer
- 2. Select set of datapath components and establish clocking methodology
- 3. Assemble datapath meeting requirements
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- 5. Assemble the control logic (hard part!)



Step 3: Assemble DataPath meeting requirements

- Register Transfer Requirements


⇒ Datapath Assembly

- Dataflow: *(Functional Union of all ISA ops)*

- Instruction Fetch IF
- Read Operands DE
- ALU Operation (if necessary) EX
- Memory Operation (if necessary) MEM
- Write back to Registers (if necessary) WB




Step 3: Abstract Implementation

 

3a: IF: Instruction Fetch


 
- The common RTL operations
 - Fetch the Instruction: $\text{mem}[\text{PC}]$
 - Update the program counter:
 - Sequential Code: $\text{PC} = \text{PC} + 4$
 - Branch and Jump: $\text{PC} = \text{"something else"}$



3a: DE: Decode (Read Operands)

• $R[rd] = R[rs] \text{ op } R[rt]$ Ex.: addU rd, rs, rt

  - Ra, Rb, and Rw come from instruction's **Rs**, **Rt**, and **Rd** fields




IF and DE are held in common for all ops.

Now, we split up behavior by op type ...





3b: Add & Subtract

 - $R[rd] = R[rs] \text{ op } R[rt]$ Ex.: addU rd, rs, rt
 - **ALUctr** and **RegWr**: control logic after decoding the instruction




• Already defined register file, ALU

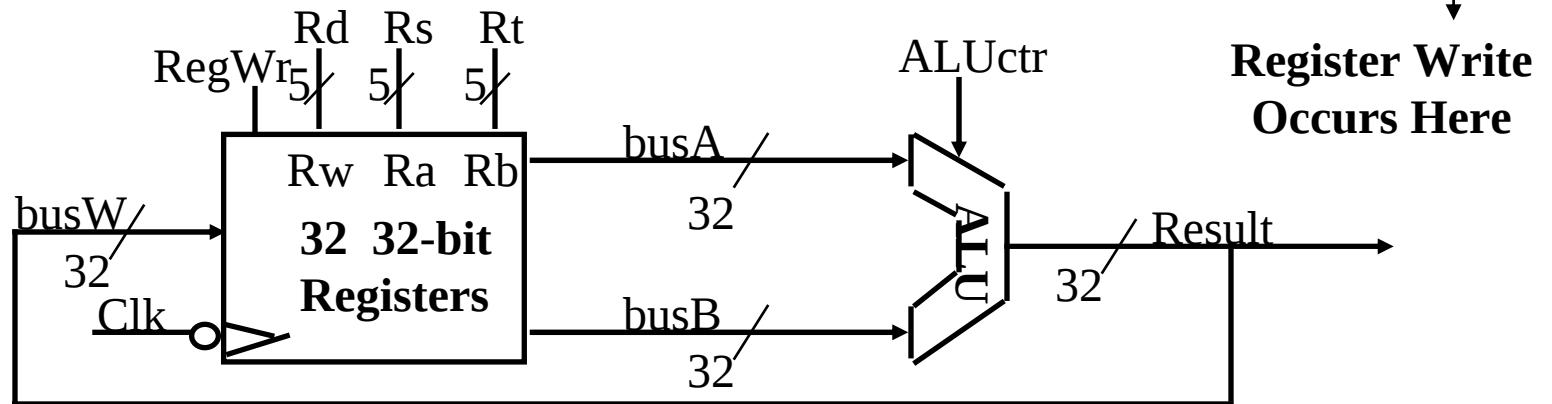 Register-Register Timing: One complete cycle



3c: Logical Operations with Immediate


 
- $R[\underline{rt}] = R[rs] \text{ op } \text{ZeroExt}[\text{imm16}]$



• Already defined 32-bit MUX; Zero Ext?


3d: Load Operations

  - $R[\underline{rt}] = \text{Mem}[R[rs] + \text{SignExt}[\text{imm16}]]$
Example: `lw rt, rs, imm16`




3e: Store Operations

 - $\text{Mem}[R[\text{rs}] + \text{SignExt}[\text{imm16}]] = R[\text{rt}]$
 Ex.: `sw rt, rs, imm16`



3f: The Branch Instruction

 


- **beq rs, rt, imm16**
 - **mem[PC]** Fetch the instruction from memory
 - **Equal = R[rs] == R[rt]** Calculate the branch condition
 - **if (Equal)** Calculate the next instruction's address
 - **PC = PC + 4 + (SignExt(imm16) x 4)**
 - else**
 - **PC = PC + 4**



Datapath for Branch Operations


- **beq rs, rt, imm16**

Datapath generates condition (equal)

 


• **Already MUX, adder, sign extend, zero**

 Putting it All Together: A Single Cycle Datapath



Recall: Clocking Methodology

 


- All storage elements are clocked by the same clock edge

• **Cycle Time** = CLK-to-Q + **Longest Delay Path** + Setup + Clock Skew




Clocking Methodology

 

- Storage elements clocked by same edge
- Being physical devices, flip-flops (FF) and combinational logic have some delays
 - Gates: delay from input change to output change
 - Signals at FF D input must be stable before active clock edge to allow signal to travel within the FF, and we have the usual clock-to-Q delay
- “Critical path” (longest path through logic) determines length of clock period

An Abstract View of the Implementation

 

An Abstract View of the Critical Path

- This affects how much you can overclock your PC!

Critical Path (Load Operation) =
Delay clock through PC (FFs) +
Instruction Memory's Access Time +
Register File's Access Time +
ALU to Perform a 32-bit Add +
Data Memory Access Time +
Stable Time for Register File Write

